

KVL in  $\Sigma$  loop -


$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$
$$15 - 2R_C - 4 - 2I_E = 0$$
$$R_C = ?$$

01/10/19

## FIELD EFFECT TRANSISTOR (FET)


Unipolar device - current flows due to majority charge carriers.  
advantages

- |   |   |
|---|---|
| ① FET $\rightarrow$ unipolar  | BJT $\rightarrow$ Bipolar.  |
| ② Input impedance of FET is very high<br>( $100 M\Omega$ )  | BJT $\rightarrow$ current controlled device.<br>( Output current changes due to change in input voltage.) |
| ③ FET $\rightarrow$ voltage controlled device.<br>( Output current changes due to change in input voltage.) |   |
| ④ FET is less noisy as compare to BJT   |   |
| ⑤ Thermal stability is better.  |   |
| ⑥ It occupies less space (during IC fabrication)  |   |

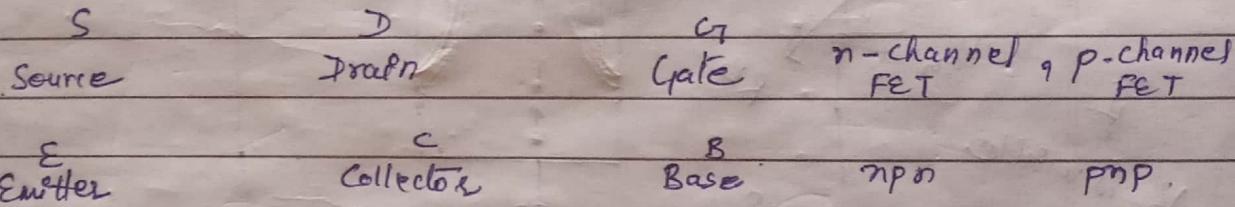

### \* Constructional Diagram of FET //


$\Rightarrow$  n-channel FET -

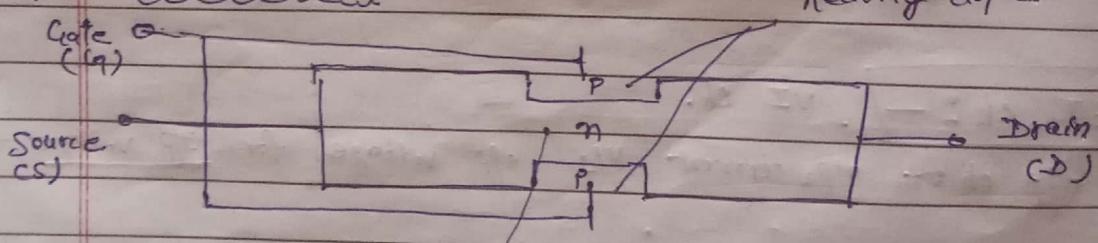

heavily doped


channel  $\rightarrow$  (space b/w 2 pn-junctions through  
GOOD WRITE which majority charge carrier passes).

\* Symbol

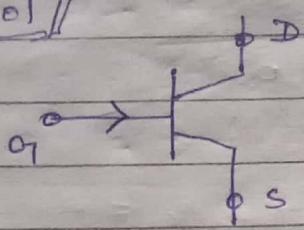

on Gate

n-channel FET

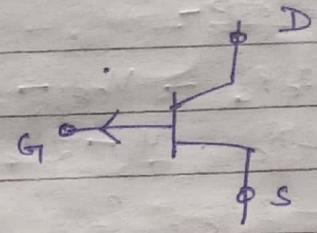


p-channel FET

Arrow shows dir<sup>n</sup> of current when GS junction is forward bias.

→ Configurations:-

→ \* Operating Principle of FETs :-

n-channel FET:-

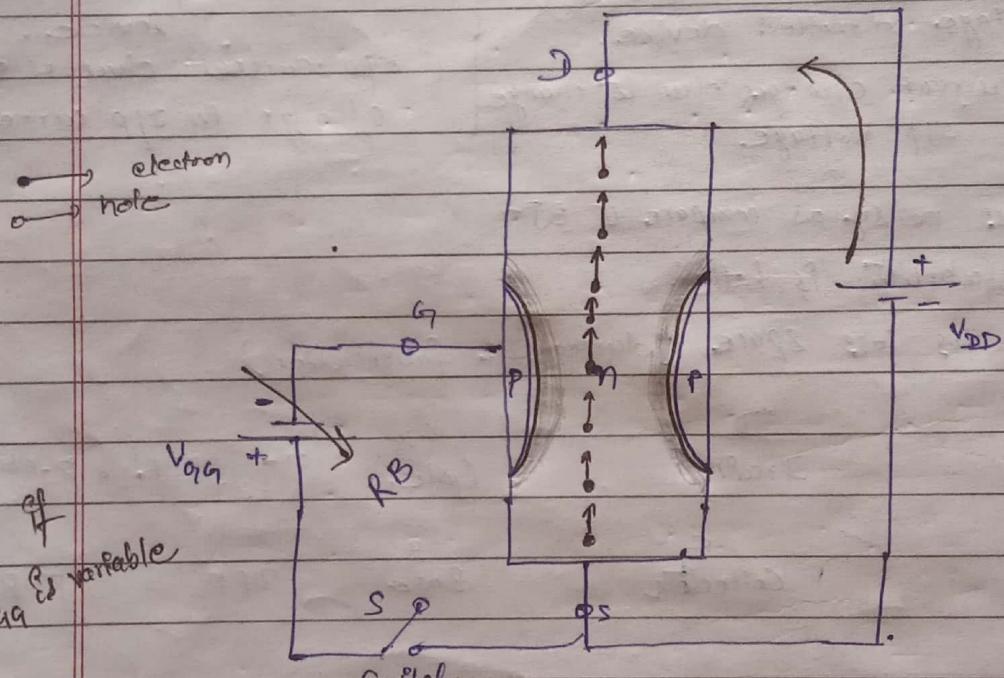

flat depletion layer will form - less majority charge carrier will enter through channel, less conduction will occurs.

⇒ External Field effect..

\* FET ch :- VI ch.

O/p ch :- o/p current v/s o/p voltage for IP voltage → const

$V_{GS} = 0 \rightarrow$  switch open.

## COMMON SOURCE

DATE: \_\_\_ / \_\_\_ / \_\_\_  
PAGE: \_\_\_

III \*

Common Source: - for n-channel FET


I/P  $\rightarrow$  Gate      O/P  $\rightarrow$  Drain      Common  $\rightarrow$  Source

O/P current  $\rightarrow$  Drain current. ( $I_D$ )

O/P voltage  $\rightarrow$  Drain to source voltage ( $V_{DS}$ )

I/P "  $\rightarrow$  Gate to source " ( $V_{GDS}$ )

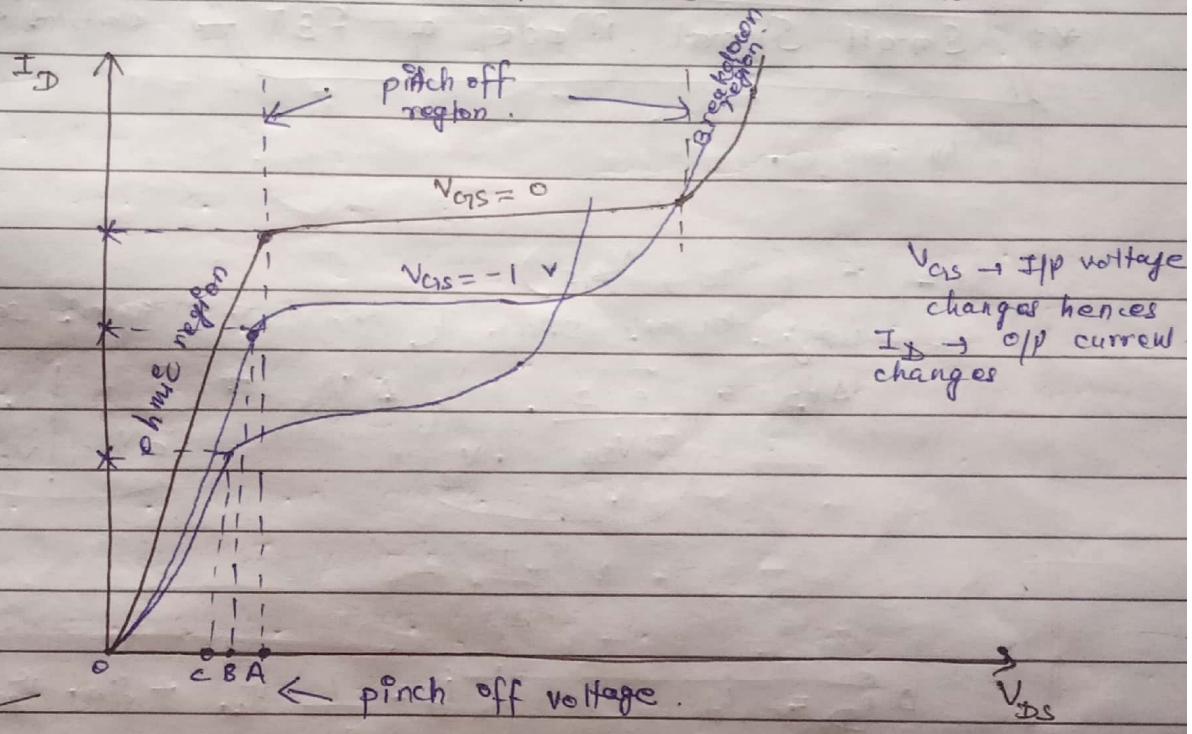O/P ch: -  $I_D$  vs  $V_{DS}$  for  $V_{GDS}$   $\rightarrow$  constant.



\* FET parameters :-

$\Rightarrow$  Common Source amplifier :-  $R_d X$

(1) ac drain resistance ( $R_d$ ) ✓

$$R_d = \frac{\Delta V_{DS}}{\Delta I_D} \quad \left| \begin{array}{l} V_{GS} = \text{constant} \\ \Delta V_{GS} = \text{zero.} \end{array} \right.$$

(2) Trans conductance ( $g_m$ )

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} \quad \left| \begin{array}{l} V_{DS} = \text{const} \end{array} \right.$$

$\frac{I}{V} \rightarrow$  O/P  
 $V \rightarrow$  I/P.

(3) Amplification factor ( $\mu$ )

GOOD WRITE

$$\mu = \frac{\Delta V_{DS}}{\Delta V_{GS}} \quad \left| \begin{array}{l} I_D = \text{const.} \end{array} \right.$$

Common  
Source amplifier.

$$\boxed{V_{DS} \quad I_D \quad V_{GS}}$$

DATE / /  
PAGE

$$\begin{aligned} m &= \frac{\Delta V_{DS}}{\Delta V_{GS}} \\ &= \frac{\Delta V_{DS}}{\Delta I_D}, \quad \frac{\Delta I_D}{\Delta V_{GS}} \\ \boxed{m = g_d \cdot g_m} \end{aligned}$$

\* Small Signal Model of FET  $\rightarrow$  detailed eq. ch. of FET

by o/p ch.

$$i_D = f(V_{DS}, V_{GS})$$

by using Taylor's series (two terms of Taylor's series)

$$\Delta i_D = \left( \frac{\partial i_D}{\partial V_{DS}} \Big|_{V_{GS}} \right) \Delta V_{DS} + \left( \frac{\partial i_D}{\partial V_{GS}} \Big|_{V_{DS}} \right) \Delta V_{GS}$$

$$\frac{1}{g_d}$$

$$g_m$$

$$\Delta i_D = i_d$$

$$\Delta V_{DS} = v_{ds}$$

$$\Delta V_{GS} = v_{gs}$$

$$i_d = \frac{1}{g_d} v_{ds} + g_m v_{gs}$$


current - current

current - current

①

KCL.


$$i_D = I_1 + I_2$$

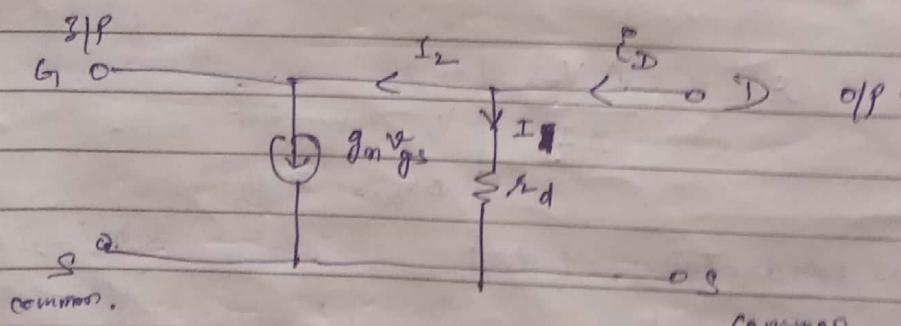

Common Source Amplifier -

I<sub>DP</sub>  $\rightarrow$  Gate

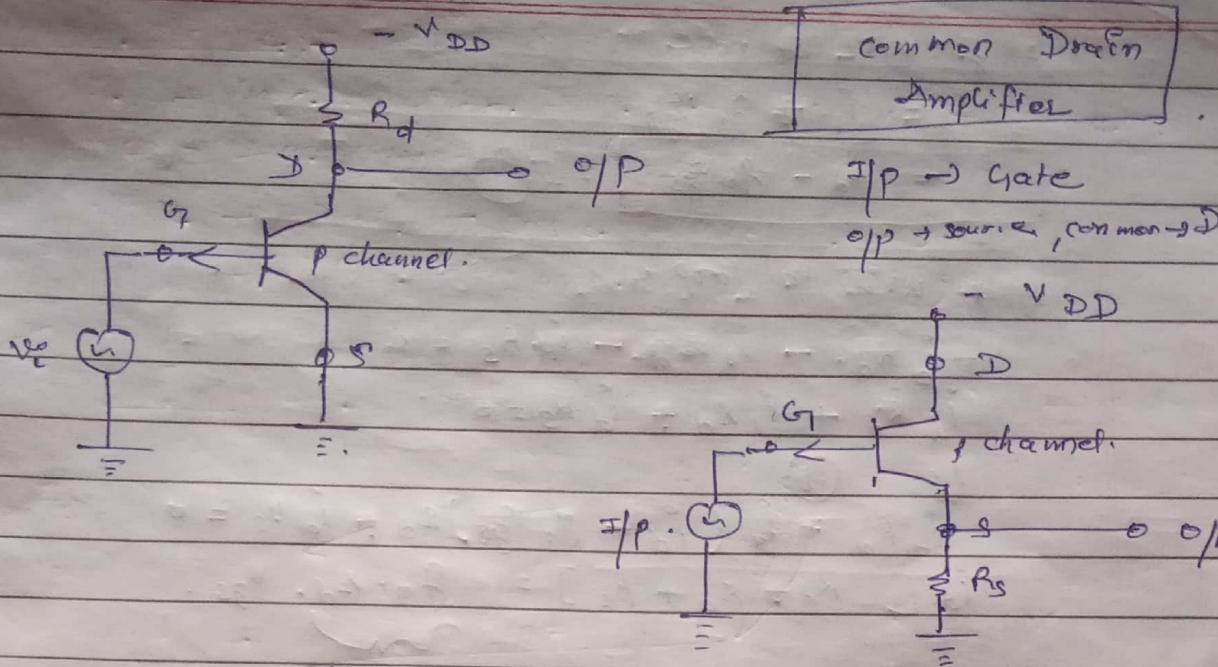GOOD WRITE P-channel  $= -V_{DD}$ , n-channel  $= +V_{DD}$ , common  $\rightarrow$  source




$\Rightarrow$  General ckt for amplifier.  $\rightarrow$  PET

If  $\sigma/\rho \rightarrow v_0$  (Darin) and  $\rho_s = 0$


then ckt  $\rightarrow$  common source amplifier.

If  $\text{S/P} \rightarrow \text{NO}_2$  (source) and  $R_d = 0$

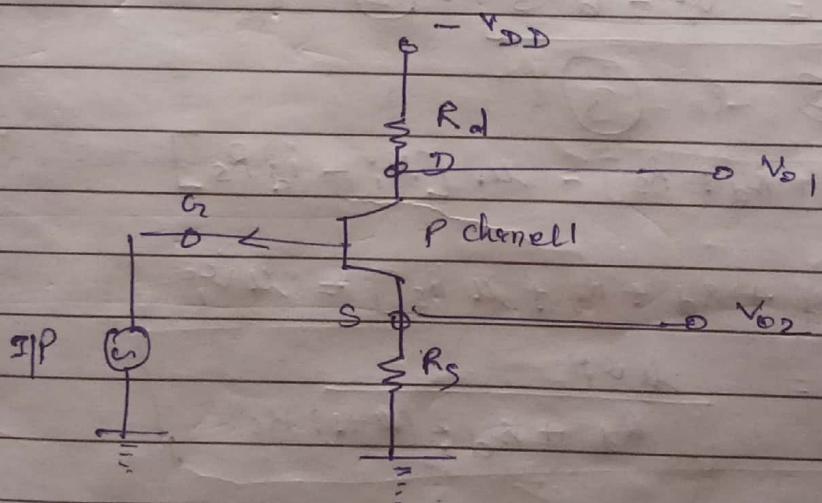then let  $\rightarrow$  common drain amplifier.



## Generalised FET amplifier ckt.

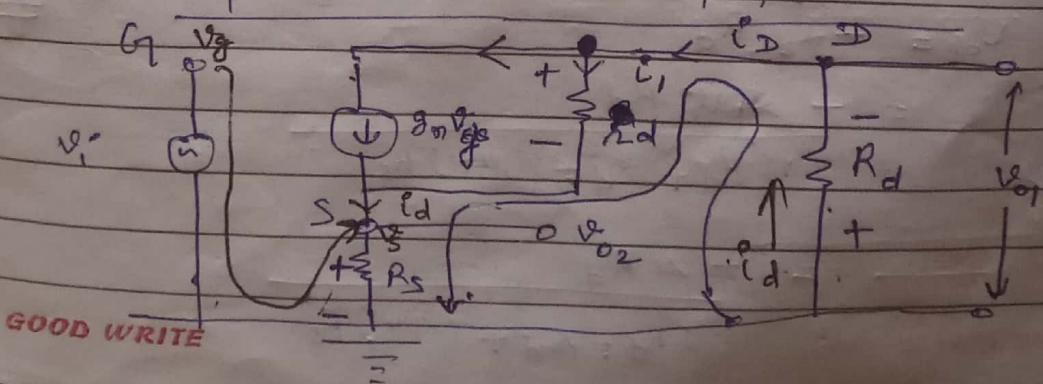

M/F/19

Apply KVL at node

$$i_d = i_1 + g_m v_{gs}$$

$$\boxed{i_1 = i_d - g_m v_{gs}} \quad \text{--- (1)}$$

Applying KVL in loop.

$$-i_d R_d - i_1 s_d - i_d R_s = 0$$

$$i_d R_d + i_1 s_d + i_d R_s = 0$$

But (1)

$$i_d R_d + \boxed{(i_d - g_m v_{gs}) s_d + i_d R_s = 0}$$

$$i_d [R_d + s_d + R_s] = \underbrace{g_m \cdot s_d \cdot v_{gs}}_{\mu}$$

$$i_d [R_d + s_d + R_s] = \mu \cdot v_{gs} \quad \text{--- (3)}$$

→ Applying KVL

$$v_g - v_i^o + i_d R_s - v_s = 0$$

$$v_g - v_s = v_i^o - i_d R_s$$

$$\boxed{v_{gs} = v_i^o - i_d R_s} \quad \text{--- (2)}$$

Put (2) in (3)

$$i_d [R_d + s_d + R_s] = \mu [v_i^o - i_d R_s]$$

$$i_d [R_d + s_d + R_s + \mu R_s] = \mu v_i^o$$

$$\boxed{i_d = \frac{\mu v_i^o}{R_d + s_d + (\mu+1) R_s}}$$

$$v_{oi} = -i_d R_d$$

$$= - \frac{\mu v_i^o R_d}{R_d + s_d + (\mu+1) R_s}$$

$$\frac{v_{oi}}{v_i^o} = - \frac{\mu R_d}{R_d + s_d + (\mu+1) R_s}$$

for common source amplifier.

$$\text{O/P} \rightarrow V_o, R_s = 0$$

$$A_v = \frac{V_{o1}}{V_i} = -\frac{\mu R_d}{R_d + R_d}$$

Voltage gain for common source amplifiers.

$$V_{o2} = I_d R_s \quad \#$$

$$V_{o2} = \frac{\mu V_i}{R_d + R_d + (\mu + 1) R_s} \cdot A_s$$

$\Rightarrow$  for common drain amplifier  $\rightarrow$  Source follower.

O/P  $\rightarrow$   $V_{o2}$  and  $R_d = 0$

$$V_{o2} = \frac{\mu V_i R_s}{R_d + (\mu + 1) A_s}$$

$$\frac{V_{o2}}{V_i} = \frac{\mu R_s}{R_d + (\mu + 1) R_s}$$

If  $(\mu + 1) R_s \gg R_d$

$$\frac{V_{o2}}{V_i} \approx \frac{\mu R_s}{(\mu + 1) R_s}$$

$$\frac{V_{o2}}{V_i} \approx \frac{\mu}{\mu + 1}$$

If  $\mu \gg 1$

$$A_v = \frac{V_{o2}}{V_i} \approx 1$$

O/P  $\rightarrow$  follows  $\rightarrow$  I/P.

$$\boxed{V_{o2} = V_i}$$

O/P is at source

so it is Source follower.

$$\boxed{A_v = \frac{V_{o2}}{V_i}}.$$

Voltage gain for common drain amplifiers.

Off ch of common source amplifier :-

In pinch off region


$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

where  $I_{DSS}$  = Drain current when gate is shorted to source

$V_{GS}$  → Voltage b/w gate & source

$V_P$  = Pinch off voltage.

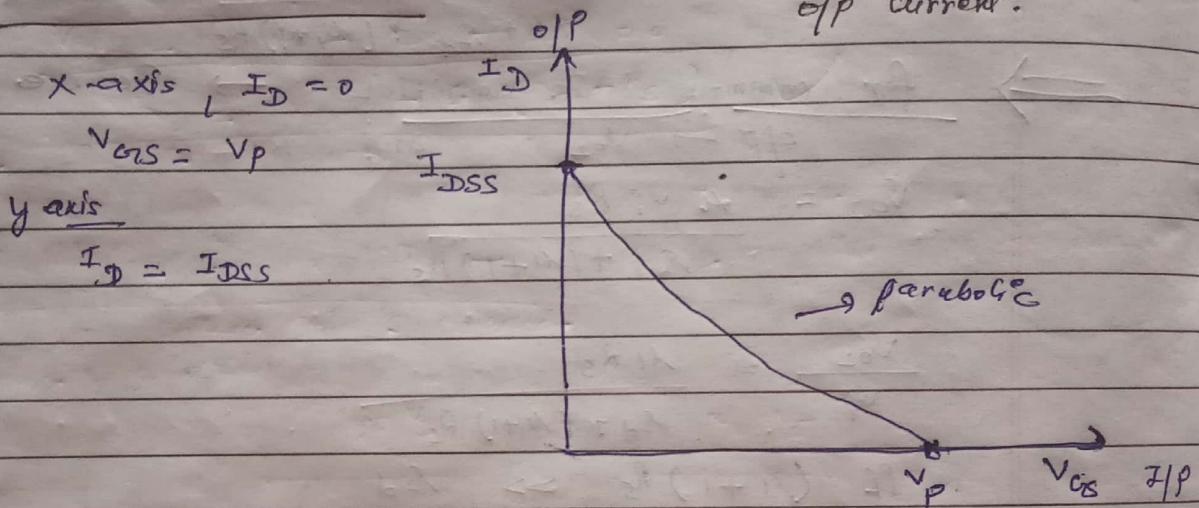
⇒ TRANSFER CH. → graph b/w I/P voltage & O/P current.



\* BIASING OF FET  
operating point  $(I_D, V_{DS})$

$$\theta = C (I_C, V_{CE})_Q$$

II ⇒ Self Bias ⇒

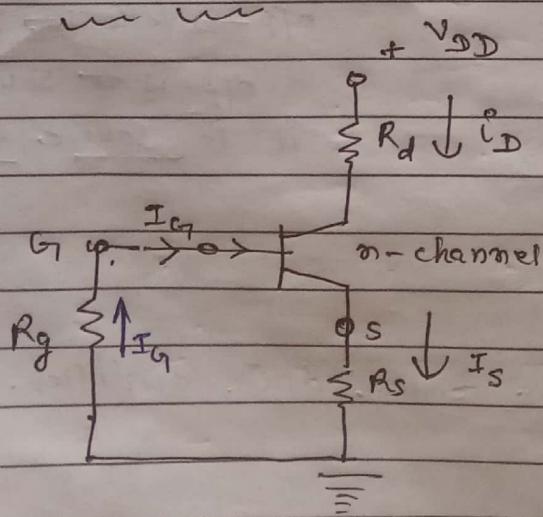

GOOD WRITE

Since gate function is Reverse biased.

$$\text{Therefore } I_g \approx 0, V_g = I_g R_s = 0$$

$$V_{GS} = V_G - V_S$$

$$= 0 - V_S$$

$$= 0 - I_s R_s$$

$$V_{GS} = 0 - I_D R_s$$

$$I_D = -\frac{V_{GS}}{R_s}$$

$$I_s \approx I_D$$

Apply KVL in o/p loop

$$V_{DD} - I_D R_d - V_{DS} - I_D R_s = 0$$



$$V_{DS} = V_{DD} - I_d (R_d + R_s)$$

⑨

// Potential Divider Biasing

Since gate function is Reverse bias

$$I_g = 0$$

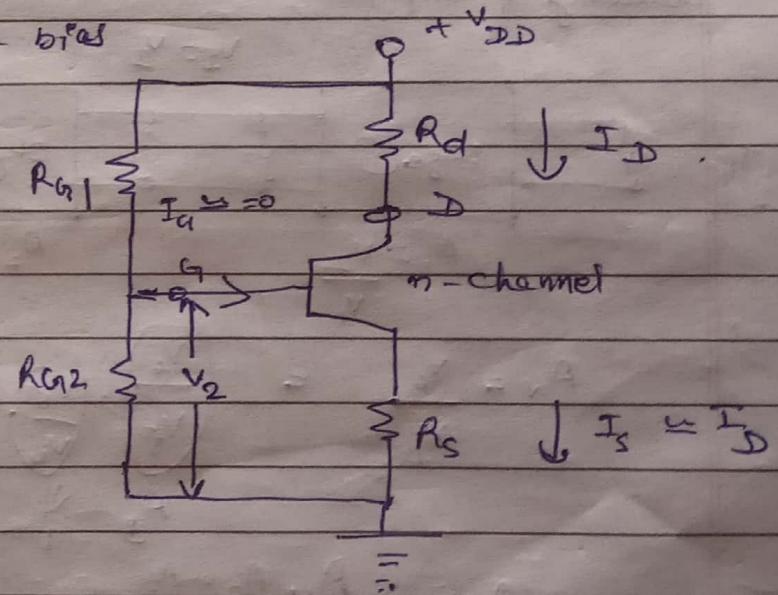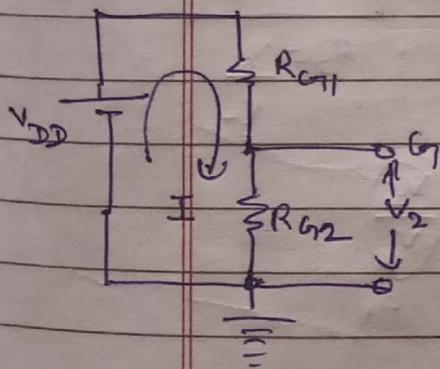

$$V_{DD} = I (R_{G1} + R_{G2})$$

$$I = \frac{V_{DD}}{R_{G1} + R_{G2}}$$

$$V_2 = I R_{G2}$$

$$V_2 = \frac{V_{DD} \cdot R_{G2}}{R_{G1} + R_{G2}} \quad \checkmark$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = V_G - I_d R_S$$

$$I_d = \frac{V_2 - V_{GS}}{R_S}$$

$$I_d = \frac{V_{DD} R_{O2}}{R_{O1} + R_{O2}} - V_{GS}$$

Apply KVL in o/p loop -

$$V_{DD} - I_d R_d - V_{DS} - I_d R_S = 0$$


$$\boxed{V_{DS} = V_{DD} - I_d (R_d + R_S)} \quad \checkmark$$

15/10/17  
\*

Multi Stage Amplifier - many amplifiers are connected.

high voltage gain is obtained.

Cascading of amplifiers:-

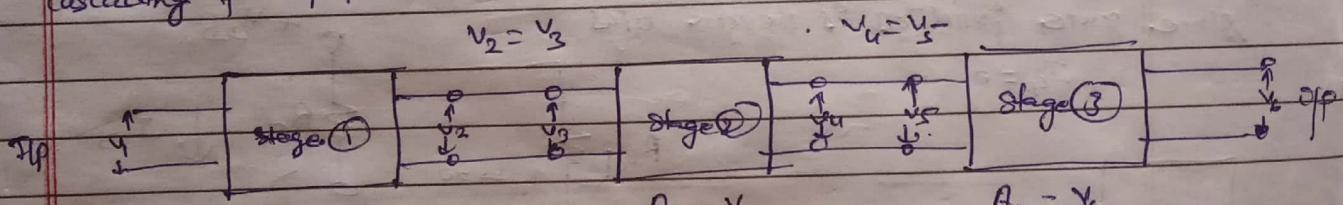

$$A_1 = \frac{V_2}{V_1}$$

$$A_2 = \frac{V_4}{V_3}$$

$$A_3 = \frac{V_6}{V_5}$$


$$A_V = \frac{V_6}{V_1} = A_1 \cdot A_2 \cdot A_3 = A_3 \cdot A_2 \cdot A_1$$

$$A_V = A_1 \cdot A_2 \cdot A_3 \dots A_n$$

only for voltage gain.

Coupling device → blocks dc, allows AC component to pass from one stage to another.

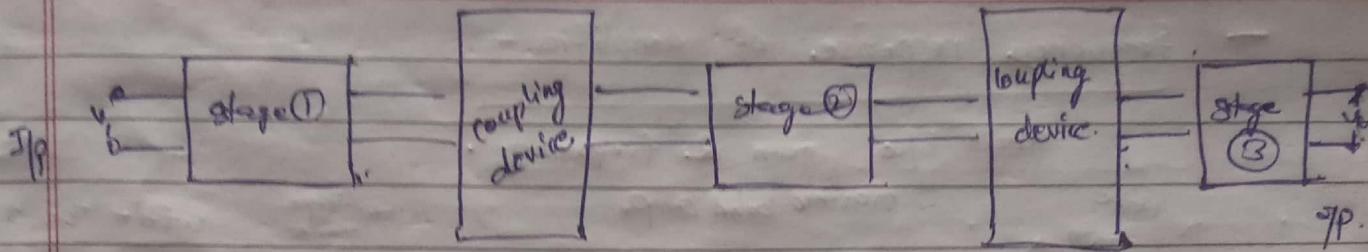Atm to block dc is to stabilize the operating points.  
bcz dc will disturb Q pt. and stability.



Device Multistage amplifier.

1. capacitor — R-C coupled amplifier.

2. Transformer — T/F " "

3. Direct — Direct " "

↓  
only for nonzero amount of dc output,  
The dc off is given at the designing time at the IIP  
of stage (another).

$$I_{bal} = \log_{10} \frac{P_{out}}{P_{in}}$$

decimal (dB)

$$\text{Power gain (1 dB)} = 10 \cdot \log_{10} \left( \frac{P_{out}}{P_{in}} \right) \rightarrow \text{Power gain.}$$

$$+ \text{decibal} + \text{decibal} = 10 \text{ bal}$$

$$\text{Voltage gain (dB)} = 20 \log_{10} \frac{V_{out}}{V_{in}}$$

$$P \propto V^2$$

$$P \propto I^2$$

$$\text{Current gain (dB)} = 20 \log_{10} \left( \frac{I_{out}}{I_{in}} \right)$$

$$\text{If Power gain} = 100, \text{ then } \underline{\text{dB}} = 10 \log_{10} 10^2 = 2 \times 10 = 20.$$

$$A_1(\text{dB}) = 20 \log_{10} A_1$$

$$A_2(\text{dB}) = 20 \log_{10} (A_2)$$

$$A_3(\text{dB}) = 20 \log_{10} (A_3)$$

$$A_V = A_1 \cdot A_2 \cdot A_3$$



$$\log_{10} A_V = \log_{10} A_1 + \log_{10} A_2 + \log_{10} A_3$$

$$20 \log_{10} A_V = 20 \log_{10} A_1 + 20 \log_{10} A_2 + 20 \log_{10} A_3$$

$$(A_V)(\text{dB}) = A_1(\text{dB}) + A_2(\text{dB}) + A_3(\text{dB})$$

- frequency response of amplifier -

graph b/w gain & frequency.

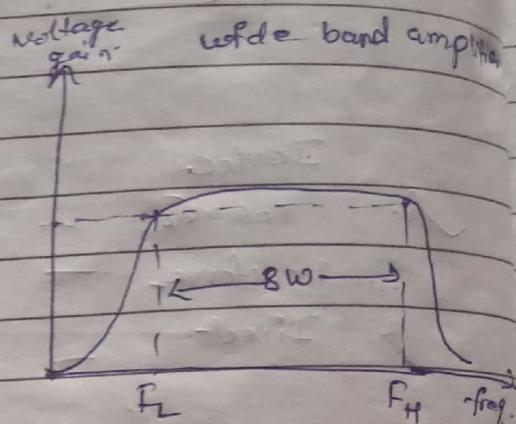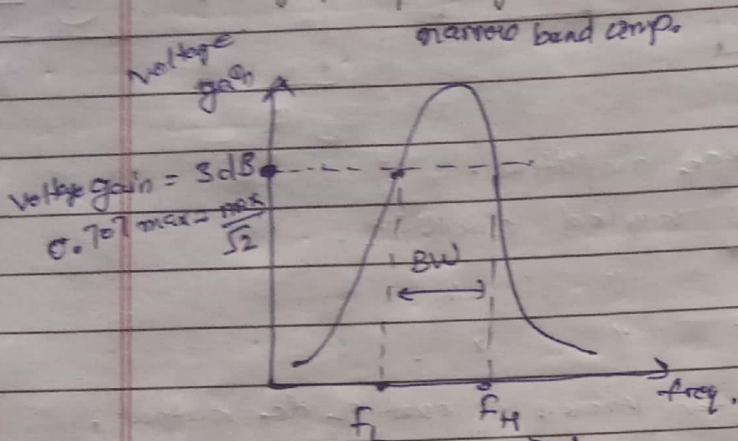

Cut off frequency  $\rightarrow$  3 dB freq  $\rightarrow$  half power freq.


$$\text{power gain} \propto V^2$$

$$\propto \left(\frac{1}{\sqrt{2}}\right)^2$$


$$\propto \frac{1}{2}$$

operational amplifier (opamp)

$\pm 12 \text{ V}$   $\pm 15 \text{ V}$

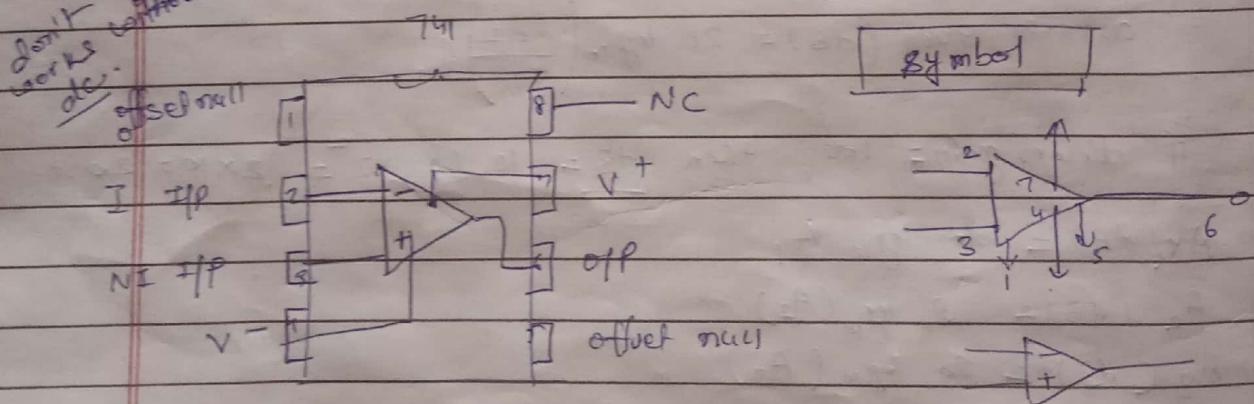

Inverting Amplifier. :-

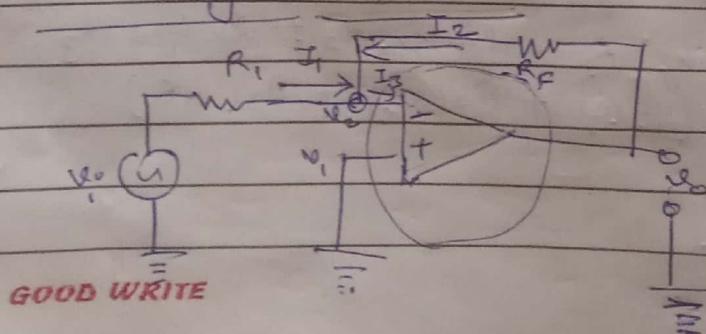

$$A_{vol} = \infty$$

$$A = \frac{V_o}{V_i - V_2} = \infty$$

Since  $V_1 = 0$   
 $V_2 = 0$

$$\left[ V_1 = V_2 \right]$$

$V_{virtual ground}$ .

Applying KCL at node pt. (2).

$$I_1 + I_2 = I_3 = 0$$

$$\frac{V_{in} - V_2}{R_1} + \frac{V_o - V_2}{R_F} = 0$$

$$\text{Since } V_1 = V_2 = 0$$

$$\frac{V_{in}}{R_1} + \frac{V_o}{R_F} = 0$$



$$\left( V_o = -\frac{R_F}{R_1} V_{in} \right) \rightarrow \text{ve due to } 180^\circ \text{ phase shift}$$

If  $R_1 = R_F$

$$\Rightarrow \text{gain} = A_v = \frac{V_o}{V_{in}} = -\frac{R_F}{R_1} \quad \left| \begin{array}{l} \checkmark [V_o = -V_{in}] \\ \text{inverter. mag. right} \end{array} \right.$$

### Non Inverting Amplifier.

more gain is obtained.

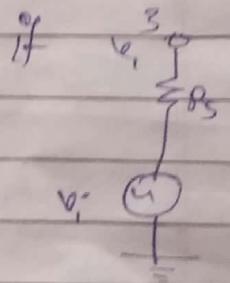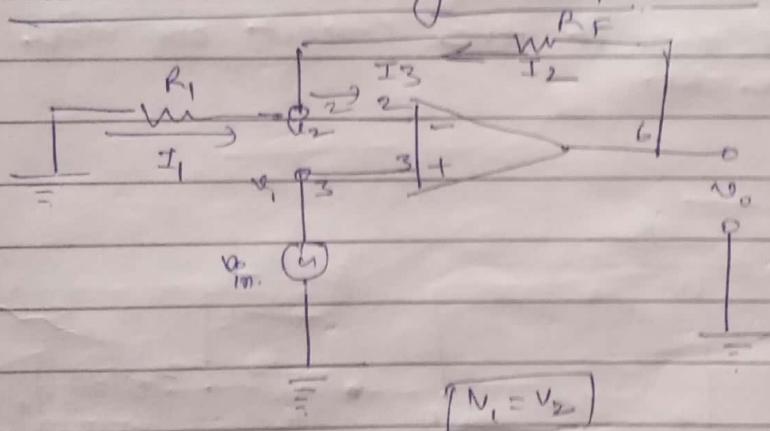

Apply KCL at pt. (2).

$$I_1 + I_2 = I_3 = 0$$

∴

$$V_1 \neq V_{in}$$

$$\left[ V_o = V_{in} \right]$$

$$0 = \frac{D}{D}$$

$$A_v = \frac{V_o}{V_{in}} = 1 + \frac{R_F}{R_1}$$

$$\begin{aligned} R_F &= \infty \\ R_1 &= 0 \\ \frac{V_o}{V_{in}} &= 1 \end{aligned}$$


GOOD WRITE

$$V_o = \left( 1 + \frac{R_F}{R_1} \right) \times \text{Voltage of NI}$$

# ⇒ ADDER

DATE \_\_\_\_\_  
PAGE \_\_\_\_\_

## (1) Inverting Adder

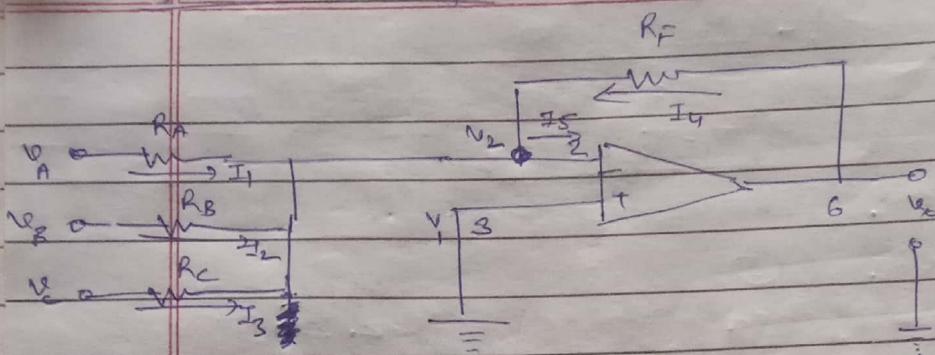

Apply KCL at pin ②

$$I_1 + I_2 + I_3 + I_4 = I_5 = 0$$

$$\frac{V_A - V_2}{R_A} + \frac{V_B - V_2}{R_B} + \frac{V_C - V_2}{R_C} + \frac{V_o - V_2}{R_F} = 0$$

since  $V_1 = V_2 = 0$

$$\frac{V_A}{R_A} + \frac{V_B}{R_B} + \frac{V_C}{R_C} + \frac{V_o}{R_F} = 0$$


$$V_o = -\frac{R_F}{R_A} V_A - \frac{R_F}{R_B} V_B - \frac{R_F}{R_C} V_C$$

if  $R_A = R_B = R_C = R_F$

$$V_o = -(V_A + V_B + V_C)$$

to make it true connect one more inverter in the ckt.

# ⇒ Subtractor

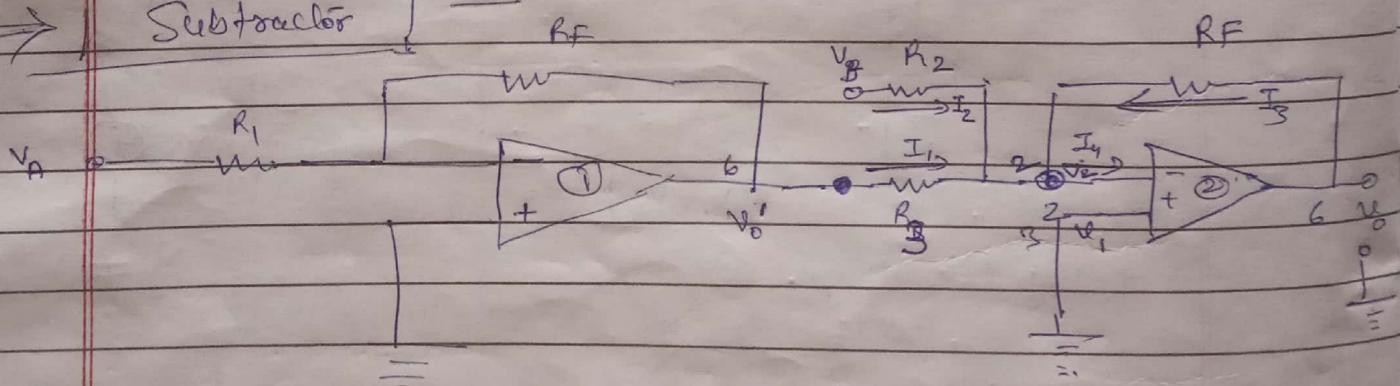

$$V'_o = -\frac{R_F}{R_1} V_A$$

Apply KCL at pin ② of opamp ②.

$$I_1 + I_2 + I_3 = I_4 = 0$$

$$\frac{V'_o - V_2}{R_3} + \frac{V_B - V_2}{R_2} + \frac{V_o - V_2}{R_F} = 0$$

GOOD WRITE

Since  $v_1 = v_2 = 0$

$$\frac{v_o'}{R_3} + \frac{v_B}{R_2} + \frac{v_o}{R_F} = 0$$

$$\frac{v_o}{R_F} = -\frac{v_o'}{R_3} - \frac{v_B}{R_2}$$

$$v_o = -\frac{R_F}{R_3} \left( -\frac{R_F}{R_1} v_A \right) - \frac{v_B}{R_2} \cdot R_F$$


$$v_o = \frac{R_F^2 v_A}{R_1 R_3} - \frac{v_B \cdot R_F}{R_2}$$

$$\text{If } R_1 = R_2 = R_3 = R_F$$

$$v_o = v_A - v_B$$

d/f must be less than 12 V.

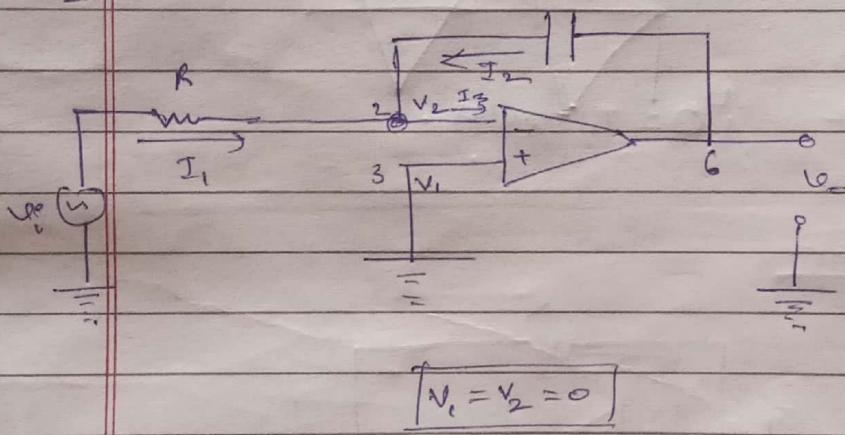$\Rightarrow$  Integrator  $\rightarrow$  adds I/P.



$$Q = CV$$

$$Q = C(v_o - v_2)$$

$$Q = Cv_o$$

$$I = \frac{dq}{dt} = C \cdot \frac{dv_o}{dt}$$

$$I_2 = C \cdot \frac{dv_o}{dt}$$

$$[v_1 = v_2 = 0]$$

Apply KCL at pt. ②

$$I_1 + I_2 = I_3 = 0$$

$$v_{in} \sim 0 + I_2 = 0$$

$$\frac{v_{in}}{R} + C \cdot \frac{dv_o}{dt} = 0$$

$$\frac{dv_o}{dt} = -\frac{1}{RC} \cdot v_{in}$$

$$v_o = -\frac{1}{RC} \int v_{in} dt$$

$$+ \int$$

GOOD WRITE




$$RC = 1 \text{ sec}$$

$$V_o = -\frac{1}{RC} \int v_i dt$$


$$-1 \cdot \int_0^{\infty} 2 dt$$

$$= -2 \left[ t \right]_0^{\infty}$$


$$V_o = -8$$

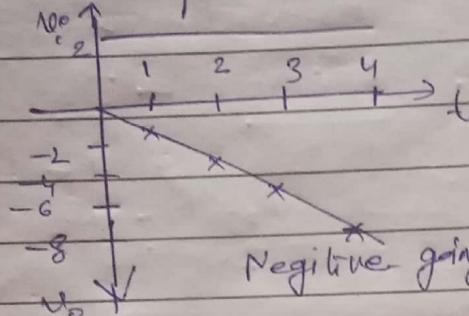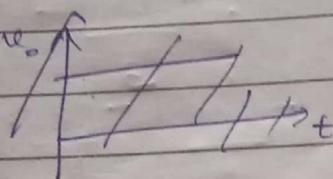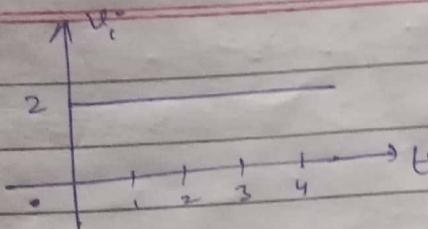

Negative going ramp.

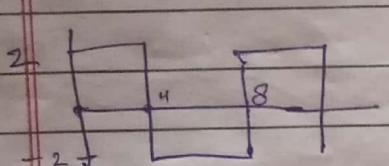


I/P = Square

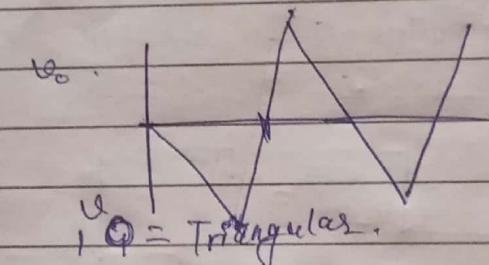

O/P = Triangular.

### Differentiator

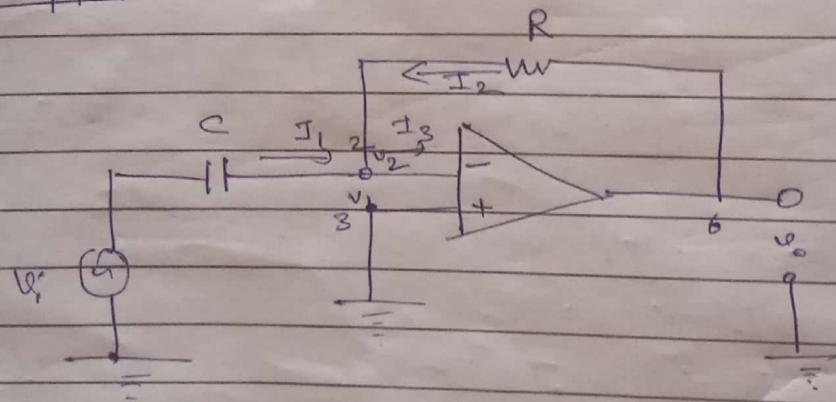

Apply KCL at (2)

$$I_1 + I_2 = I_3 = 0$$


$$V_1 = 0, \quad V_2 = 0$$

$$C \frac{d(V_i - V_2)}{dt} + \frac{V_o - V_2}{R} = 0$$

$$C \cdot \frac{dV_i}{dt} + \frac{V_o}{R} = 0$$

$$\boxed{v_o = -RC \cdot \frac{dv_i}{dt}}$$

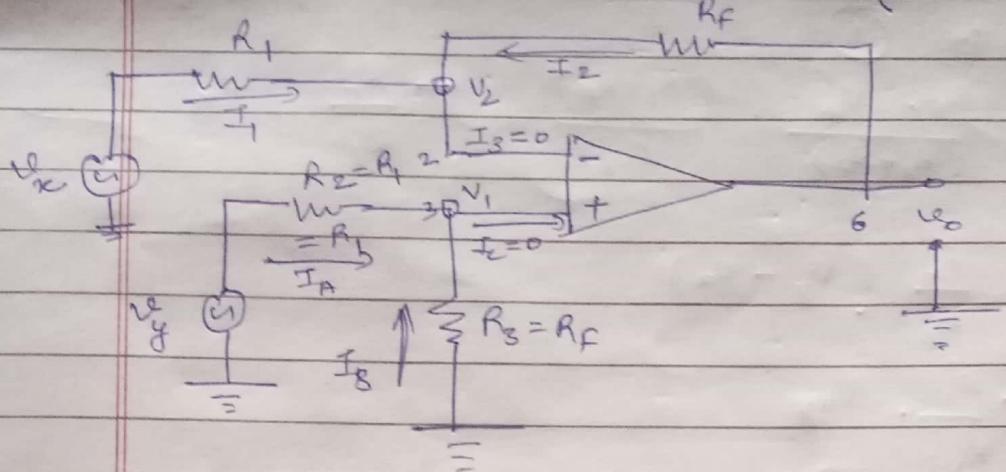$\Rightarrow$  Differential Amplifier (using opamp)  $\rightarrow$  one opamp



Since  $v_1 = v_2$ .

Apply KCL at pin ②.

$$I_1 + I_2 = 0$$

$$\frac{v_x - v_2}{R_1} + \frac{v_o - v_2}{R_f} = 0$$

Since  $v_2 = v_1$ ,

$$\frac{v_x - v_1}{R_1} + \frac{v_o - v_1}{R_f} = 0$$

$$\frac{v_x}{R_1} + \frac{v_o}{R_f} = v_1 \left( \frac{1}{R_1} + \frac{1}{R_f} \right)$$

$$\frac{v_x}{R_1} + \frac{v_o}{R_f} = v_1 \left( \frac{R_1 + R_f}{R_1 R_f} \right)$$

$$v_o = v_1 \left( \frac{R_1 + R_f}{R_1} \right) - \frac{R_f}{R_1} v_x$$

✓ ①

Apply KCL at pin ③

$$I_A + I_B = 0$$

$$\frac{v_y - v_1}{R_1} + \frac{0 - v_1}{R_f} = 0$$

$$\frac{v_y}{R_1} = \frac{v_1}{R_1} + \frac{v_1}{R_f}$$

GOOD WRITE

$$\frac{V_y}{R_1} = V_1 \left( \frac{R_1 + R_F}{R_1 R_F} \right)$$

$$V_1 = \frac{R_F}{R_1 + R_F} \cdot V_y$$

Put in ①


$$V_o = \frac{R_F \cdot V_y}{(R_1 + R_F)} \cdot \frac{(R_1 + R_F)}{R_1} - \frac{R_F}{R_1} \cdot V_x$$

$$V_o = \frac{R_F}{R_1} (V_y - V_x)$$

$$V_o = - \frac{R_F}{R_1} \cdot V_{xy}$$

$$\text{gain} = \frac{V_o}{V_{xy}} = - \frac{R_F}{R_1}$$

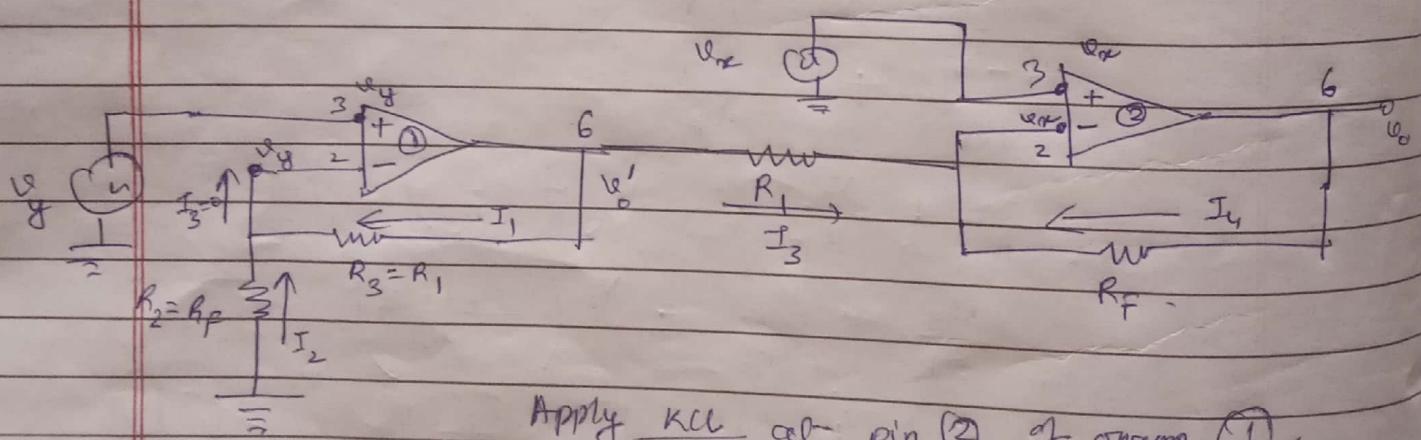$\Rightarrow$  Differential Amplifier using two opamps



Apply KCL at pin ② of opamp ①.

$$I_1 + I_2 = I_3 \approx 0$$

$$\frac{V_o' - V_y}{R_1} + 0 - \frac{V_y}{R_F} = 0$$

$$\frac{V_o'}{R_1} = \frac{V_y}{R_1} + \frac{V_y}{R_F}$$

$$V_o' = V_y \left( \frac{R_1 + R_F}{R_F} \right)$$

$$V_o' = V_y \left( 1 + \frac{R_1}{R_F} \right)$$

GOOD WRITE

34

Apply KCL at pin (2) of opamp (2)

$$I_3 + I_u = 0$$

$$\frac{V_o' - V_x}{R_i} + \frac{V_o - V_x}{R_F} = 0$$

$$\frac{V_o'}{R_i} + \frac{V_o}{R_F} = V_x \left( \frac{R_i + R_F}{R_i R_F} \right)$$

$$\frac{V_o}{A_F} = V_x \left( \frac{R_i + R_F}{R_i R_F} \right) - \frac{V_o'}{R_i}$$

$$V_o = V_x \left( \frac{R_i + R_F}{R_i} \right) - \frac{R_F}{R_i} V_o'$$

$$V_o = \frac{V_x (R_i + R_F)}{R_i} - \frac{R_F}{R_i} \cdot V_y \left( \frac{A_F + R_i}{R_F} \right)$$

$$V_o = \frac{R_i + R_F}{R_i} [V_x - V_y]$$

$$V_o = \left( 1 + \frac{R_F}{R_i} \right) (V_{xy})$$

$$\text{gain} = \frac{V_o}{V_{xy}} = 1 + \frac{R_F}{R_i}$$

9/34  
Apply KCL at pin ② of opamp ②

$$I_3 + I_4 = 0$$

$$\frac{V_o' - V_x}{R_i} + \frac{V_o - V_x}{R_F} = 0$$

$$\frac{V_o'}{R_i} + \frac{V_o}{R_F} = V_x \left( \frac{R_i + R_F}{R_i R_F} \right)$$

$$\frac{V_o}{A_F} = V_x \left( \frac{R_i + R_F}{R_i R_F} \right) - \frac{V_o'}{R_i}$$

$$V_o = V_x \left( \frac{R_i + R_F}{R_i} \right) - \frac{R_F}{R_i} V_o'$$

$$V_o = \frac{V_x (R_i + R_F)}{R_i} - \frac{R_F}{R_i} V_{xy} \left( \frac{R_F + R_i}{R_F} \right)$$


$$V_o = \frac{R_i + R_F}{R_i} [V_x - V_{xy}]$$

$$V_o = \left( 1 + \frac{R_F}{R_i} \right) (V_x - V_{xy})$$

$$\text{gain} = \frac{V_o}{V_{xy}} = 1 + \frac{R_F}{R_i}$$

~~on 11/15~~

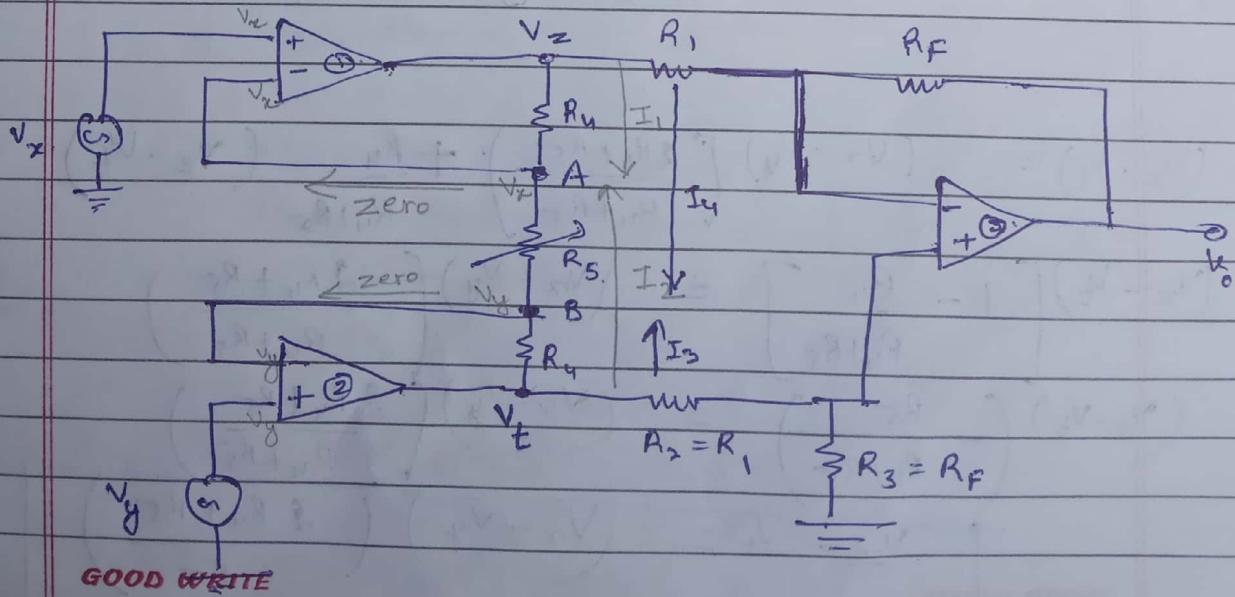\* Differential Amplifier using three opamps.



GOOD WRITE

Apply KCL at A

$$I_1 + I_2 = 0$$

$$\frac{V_z - V_x}{R_y} + \frac{V_t - V_x}{R_u + R_5} = 0$$

$$\frac{V_z}{R_y} = \frac{V_x}{R_u} - \frac{V_t}{R_u + R_5} + \frac{V_x}{R_u + R_5}$$

$$\frac{V_z}{R_y} = V_x \left[ \frac{2R_u + R_5}{R_u(R_u + R_5)} \right] - \frac{V_t}{R_u + R_5}$$

$$V_z = V_x \left[ \frac{2R_u + R_5}{R_u + R_5} \right] - \frac{R_u V_t}{R_u + R_5}$$

Apply KCL at B

$$I_3 + I_4 = 0$$

$$\frac{V_t - V_y}{R_u} + \frac{V_z - V_y}{R_u + R_5} = 0$$

$$\frac{V_t}{R_u} = \frac{V_y}{R_u} - \frac{V_z}{R_u + R_5} + \frac{V_y}{R_u + R_5}$$

$$\frac{V_t}{R_u} = V_y \left[ \frac{2R_u + R_5}{R_u(R_u + R_5)} \right] - \frac{V_z}{R_u + R_5}$$

$$V_t = V_y \left[ \frac{2R_u + R_5}{R_u + R_5} \right] - \frac{R_u V_z}{R_u + R_5}$$

$$(V_z - V_t) = (V_x - V_y) \left( \frac{2R_u + R_5}{R_u + R_5} \right) + \frac{R_u}{R_u + R_5} (V_z - V_t)$$

$$(V_z - V_t) \left[ 1 - \frac{R_u}{R_u + R_5} \right] = (V_x - V_y) \left( \frac{2R_u + R_5}{R_u + R_5} \right)$$

$$(V_z - V_t) \left( \frac{R_5}{R_u + R_5} \right) = (V_x - V_y) \left( \frac{2R_u + R_5}{R_u + R_5} \right)$$

GOOD WRITE

$$V_z - V_t = (V_x - V_y) \left( \frac{2R_u + R_5}{R_5} \right)$$

using  $\text{PDT}$ 

II

Input of  
(V<sub>in</sub>)

$$V_{Zt} = \frac{2(R_u + R_f)}{R_f} \cdot V_{xy}$$

using ~~pop up P~~

$$V_o = -\frac{R_f}{R_i} (V_Z - V_t)$$

$$V_o = -\frac{R_f}{R_i} \left( \frac{2(R_u + R_f)}{R_f} \right) V_{xy}$$


$$\text{gain} \quad \frac{V_o}{V_{xy}} = -\frac{R_f}{R_i} \left( \frac{2(R_u + R_f)}{R_f} \right) = -\frac{R_f}{R_i} \left( 1 + \frac{2R_u}{R_f} \right)$$

$\Rightarrow$  [ offset Error voltage and current.  $\rightarrow$  ]


due to internal mismatching of transistors inside the IC.

Input offset voltage ( $V_{io}$ )

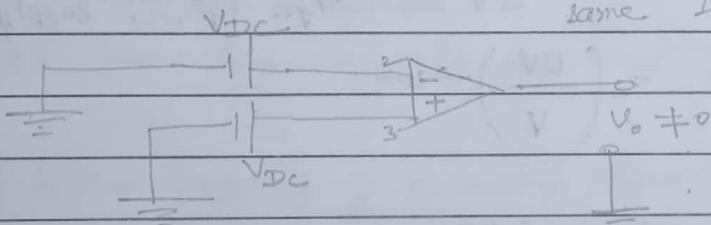I1  
  
input offset voltage  
( $V_{io}$ )



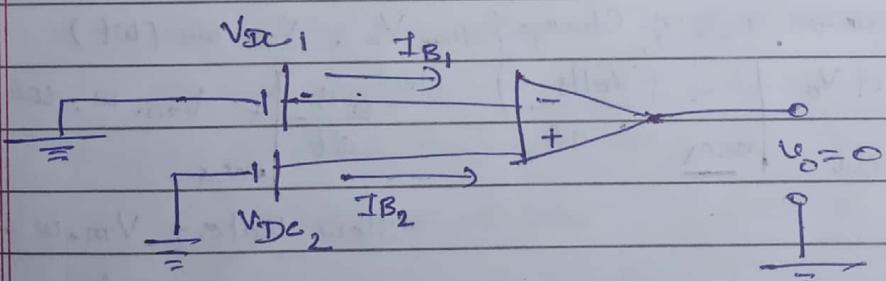same IIP dc, the off should be zero but it's not due to error



$$V_{io} = V_{DC_1} - V_{DC_2}$$

Input offset voltage

I2  
input offset current ( $I_{io}$ )


$$I_{io} = |IB_1 - IB_2| \Big|_{V_o = 0}$$

I3  
Input bias current -

$$I_B = \frac{IB_1 + IB_2}{2}$$

### [4] o/p offset voltage ( $V_o$ )

DC is not zero.

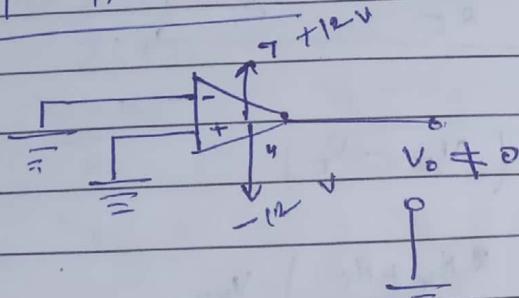

Input voltages are zero but o/p is not zero.

To make o/p offset voltage zero, we use pins 2, 4 and 5. Resistor is placed b/w 1 & 5.

### [5] Supply Voltage Rejection Ratio (SVRR)

Power supply Rejection Ratio (PSRR).

$$SVRR = \frac{\Delta V_{io}}{\Delta V} \rightarrow \text{change in input offset voltage}$$

$\Delta V \rightarrow \text{change in dc supply voltage}$

$$SVRR = \left( \frac{UV}{V} \right) \rightarrow \text{unit: } \frac{\text{Volts}}{\text{Volts}}$$

### [6] Slew Ratio (SR)

maximum rate of change of voltage  $V_o = V_m \sin(\omega t)$

$$SR = \frac{dV_o}{dt} \Big|_{\text{max}} = \left( \frac{\text{Volts}}{\mu\text{s}} \right) \quad Slew = \frac{dV_o}{dt} \Big|_{\text{max}} = V_m \cdot \omega \cdot 0.08 \omega t \Big|_{\text{max}}$$

$$\begin{aligned} \text{Slew Rate} &= V_m \cdot \omega = V_m 2\pi f \\ &= V_m 2\pi f \quad \text{Volts/sec} \end{aligned}$$

### [7] Common Mode Rejection Ratio (CMRR)

It is a ratio of differential gain of an opamp to the common mode gain.

$$CMRR = \frac{\text{differential Gain (A_d)}}{\text{common Mode gain (A_c)}} = \frac{A_d}{A_c}$$

gain when same AC signal is applied at both Inverting & non-inverting terminal ( $V_{cm}$ )

$$A_C = \frac{V_{out}}{V_{in}} = \boxed{dB}$$

for an ideal opamp  $V_{out} = 0$ ,

$$\Rightarrow A_C = 0$$

ideally, CMRR =  $\infty$

practically • CMRR  $\rightarrow$  very large  $\rightarrow$  very good opamp.

$\Rightarrow$  OSCILLATORS — converts DC into AC.

is a ckt that generates a repetitive waveform of fixed amplitude & without giving any external AC signal source. (means AC is not given)  
but DC is given.

e.g. → CRO.

$\Rightarrow$  Classification of oscillator —

I. According to wave shape of generated signal  $\Rightarrow$   
oscillator. ← (a) Sineoidal oscillators. → sine wave is generated  
waveform generator ← (b) Non-sineoidal oscillators. → square wave, triangular wave

II. According to the frequency of generated signal  $\Rightarrow$

(a) Audio generator oscillator. (few Hz - 20 kHz)

(b) Radio freq. oscillator (20 kHz - 30 MHz)

(c) Very high freq. " (30 MHz - 20 GHz)

(d) Ultra high freq. oscill. (UHF) (300 MHz - 3 GHz)

(e) Microwave oscillator (3 GHz - several GHz)

III. According to the type of components used in ckt.  $\rightarrow$

Radio  $\begin{cases} \text{a)} \\ \text{b)} \end{cases}$  LC oscillator.  $\rightarrow$  e.g. Hartley oscillator, Colpitt's oscillator


Radio  $\begin{cases} \text{a)} \\ \text{b)} \end{cases}$  RC "  $\rightarrow$  e.g. R.C. phase shift oscillator, Wein Bridge oscillator.

(c) Crystal oscillator.  $\rightarrow$  wrist watch, cars.  
↳ used for stabilization.

Sinusoidal oscillator.

+ve feedback's app<sup>n</sup> → oscillator.

(A) gain without feedback

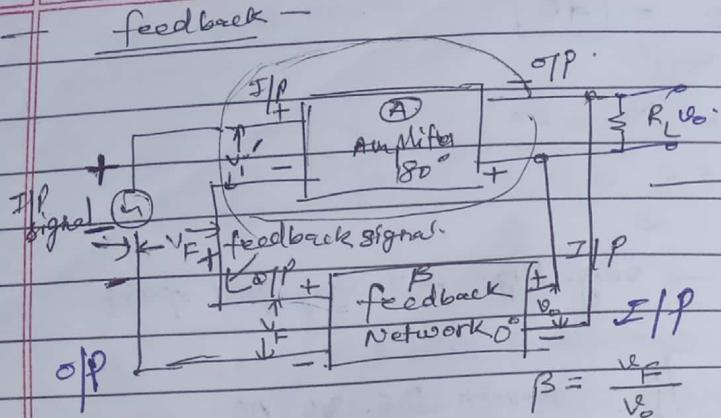

(2)

feedback  
Netw

180  
P.

+ve feedback  $\leftarrow A_F = \frac{V_o}{V_i} = \frac{A}{1 + A\beta}$

→ +ve feedback. → behavior as oscillator when  $A\beta = 1$


$$V_i = V_i + V_F$$

Amp  $\rightarrow 0^\circ$   
feedback Network  $\rightarrow 0^\circ$

$$V_i = V_i + \beta V_o$$

$$A = \frac{V_o}{V_i + \beta V_o}$$
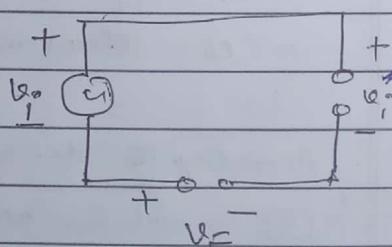
$$A_F = \frac{V_o}{V_i} = \frac{A}{1 - A\beta}$$



$A\beta = \text{loop gain.}$

$$A_F = \frac{V_o}{V_i} = \frac{A}{1 - A\beta}$$

If  $A\beta = 1$

$$\frac{V_o}{V_i} = \frac{A}{1 - A\beta} = \infty$$

GOOD WRITE

when  $V_i = 0$

$A_F = \infty$  def not oscillatory

2

using  $60^\circ$   
feedback

Input is  
Capacitor.  
 $R \rightarrow \text{out}$

polar form  $AB = \textcircled{1} L 0^\circ \text{ or } 360^\circ$   
 magnitude


This is called Barkhausen Criteria of oscillator.

two requirements for oscillations —

- (1) The magnitude of loop gain ( $AB$ ) must be at least 1
- (2) The total phase shift of loop gain " " equals  $0^\circ$  or  $360^\circ$

### \* AC . phase Shift Oscillator / -

⇒ Phase shift Network (using RC) →

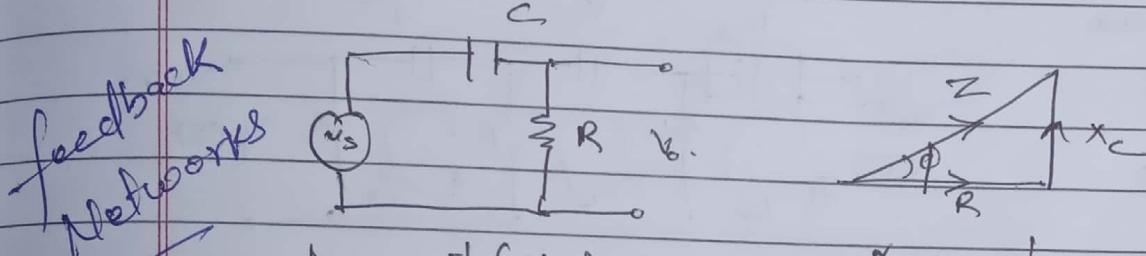

feedback  
Networks

$$\phi = \tan^{-1} \left( \frac{x_c}{R} \right)$$

$$x_c = \frac{1}{2\pi f C}$$


$$|Z| = \sqrt{R^2 + x_c^2}$$

$$\phi = \tan^{-1} \left( \frac{1}{2\pi f C R} \right)$$

$$\tan(180^\circ) = \frac{1}{2\pi f R C} = 0$$

very large practically not possible.

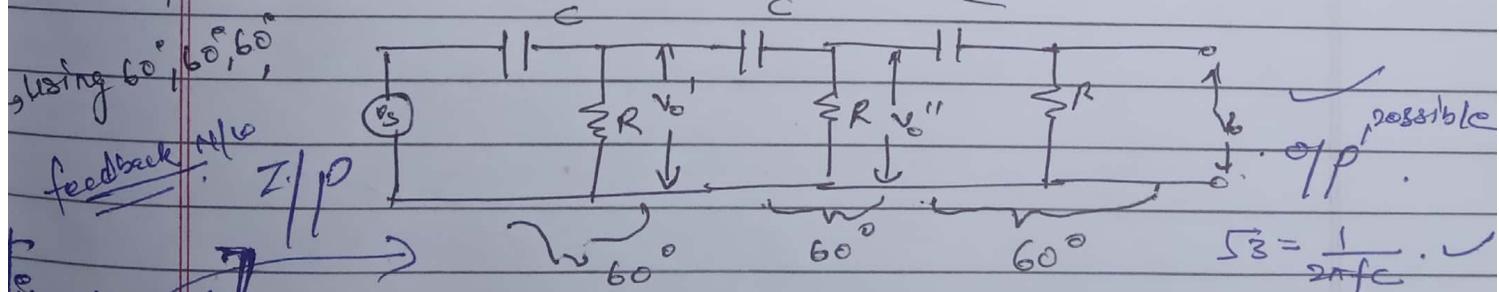
if each  $90^\circ$  and  $90^\circ = 180^\circ \rightarrow \frac{1}{2\pi f C} = \infty \rightarrow \text{same}$



Input is at capacitor. / RC phase shift oscillator using opamp: - /

R → output

No ac source

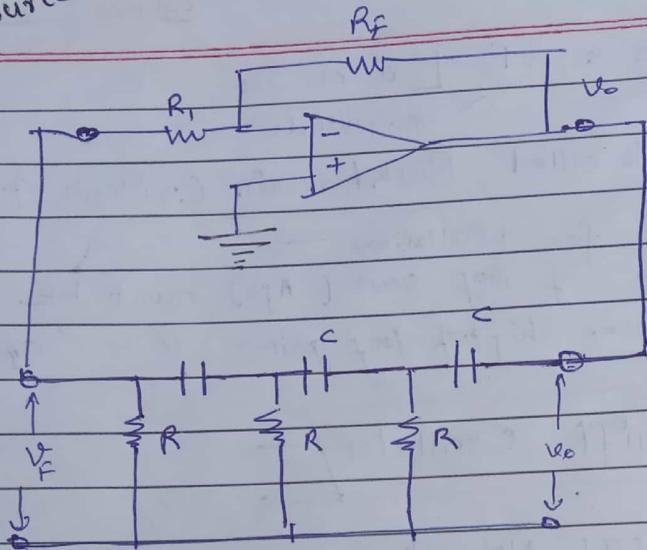


components. replace

$$C \frac{1}{CS}$$

$$L S$$

$$R$$

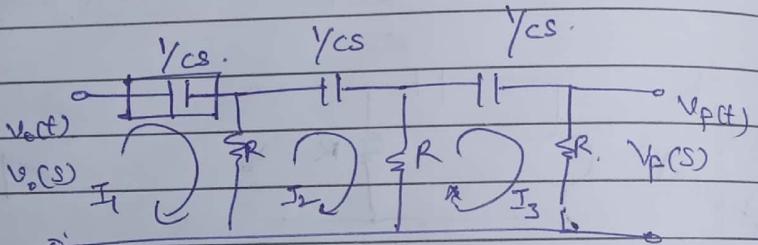

$$\text{Voltage} = I_1 \cdot \frac{1}{CS}$$

$$\text{find } \frac{V_p(s)}{V_o(s)} =$$

18/11/17

Converter !!

→ works in saturation region.

DATE: \_\_\_/\_\_\_/\_\_\_  
PAGE \_\_\_

Inverting  
NI → Non Inverting

COMPARATOR :- using opamp.


If  $NI > I$

op →  $+V_{sat}$

If  $NI < I$

op →  $-V_{sat}$ .



opamp. Transfer ch.

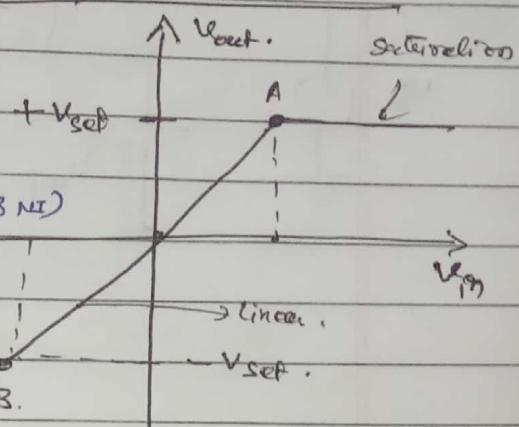

Non-inverting comparator - if  $V_{in}$  is at  $I$  (pin 3 NI)

$V_{ref} < V_{in}$



1.

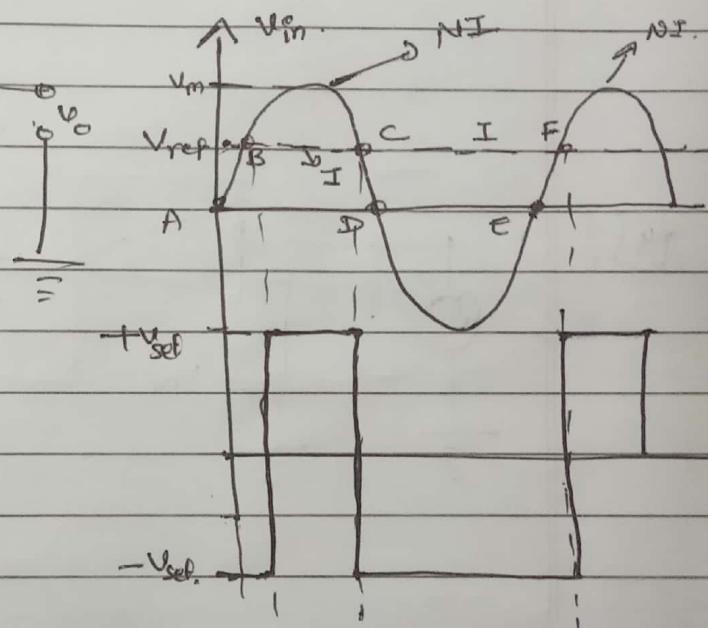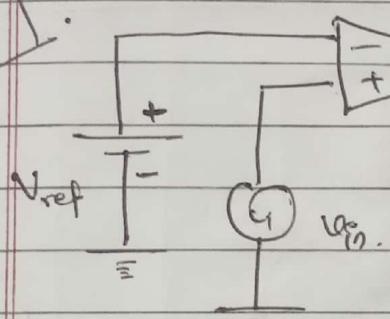

$T_{off} \rightarrow T_{on}$

→ rectangular wave form

2.

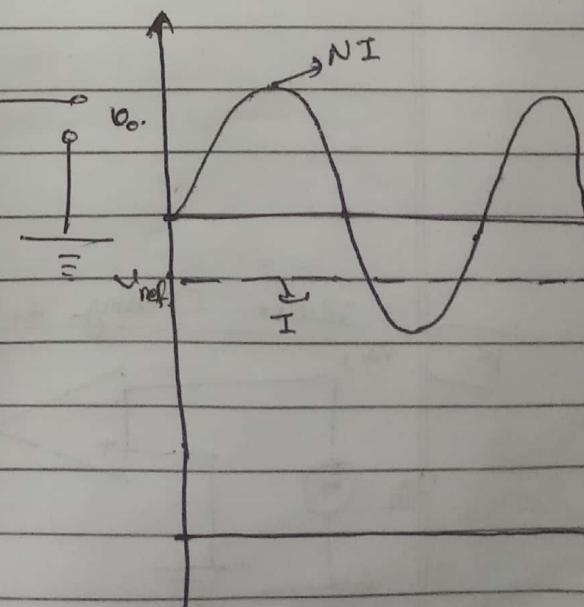
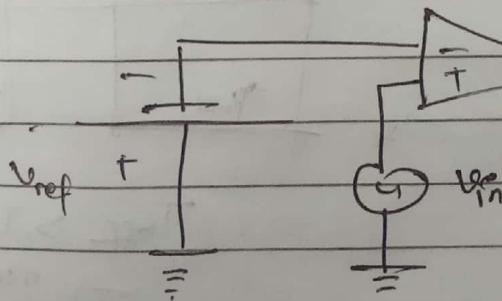


# Converter



ref generator

DATE: / /  
PAGE

$V_C$  comparators

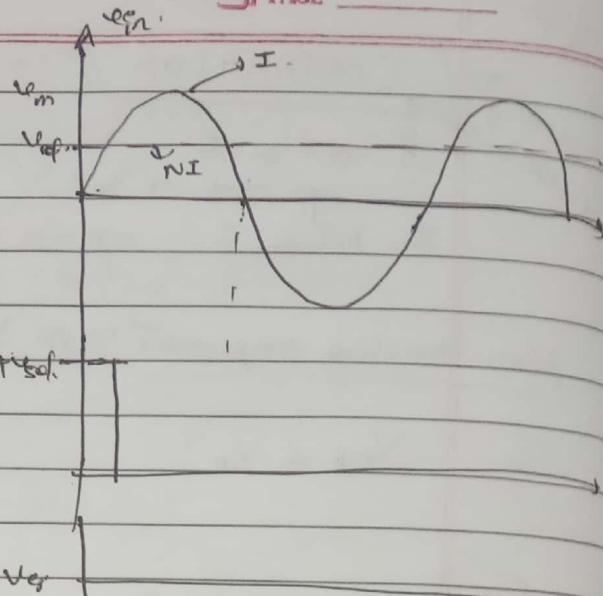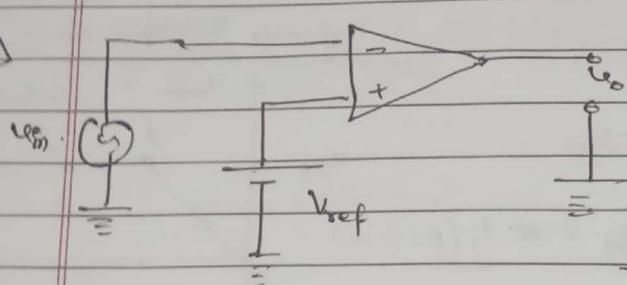



T4.

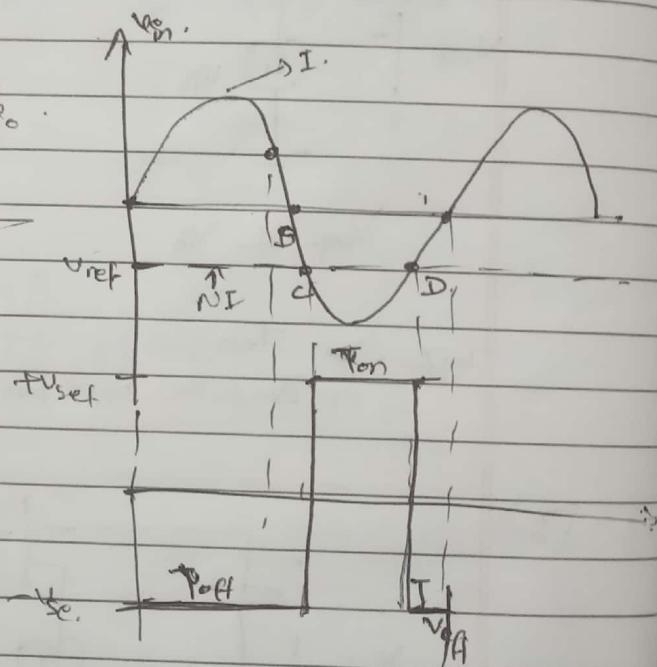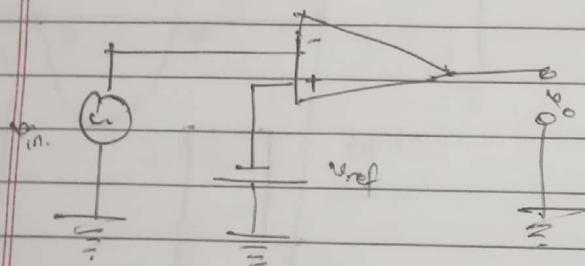

Zero crossing detector:

$T_{off} > T_{on}$

→ rectangular

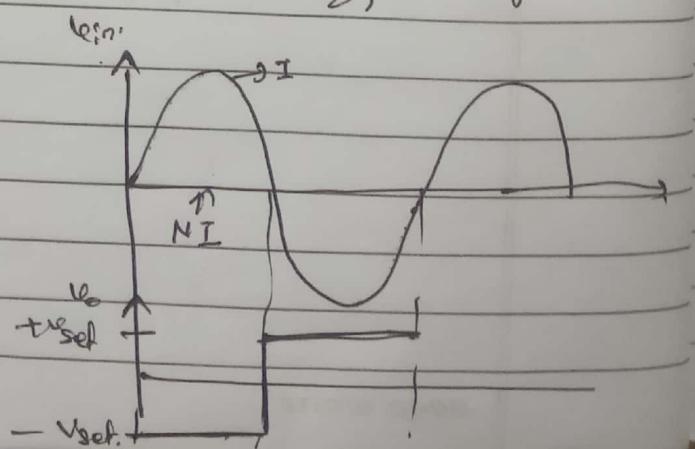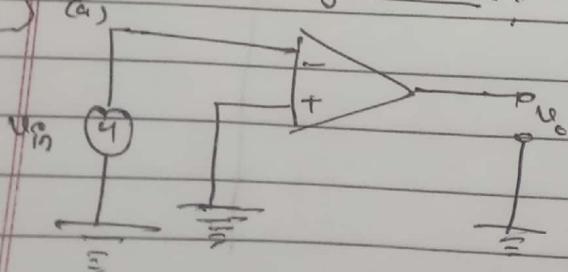



GOOD WRITE

Square waves  
is obtained

Comparator


$V_o$  is crossing the zero at the zero of the input.

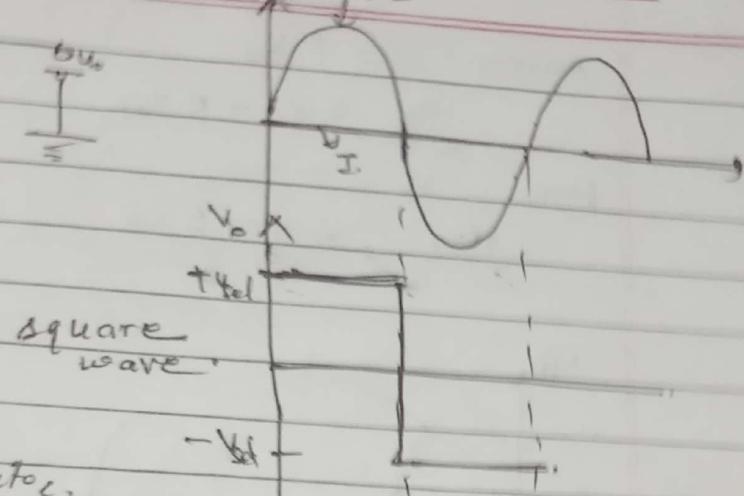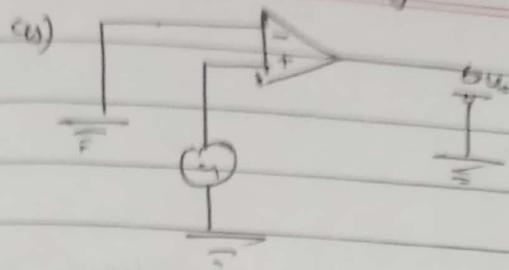↓ zero crossing detector using the ~~opamp~~ Net generator.



Hysteresis comparator.

Schmitt trigger:

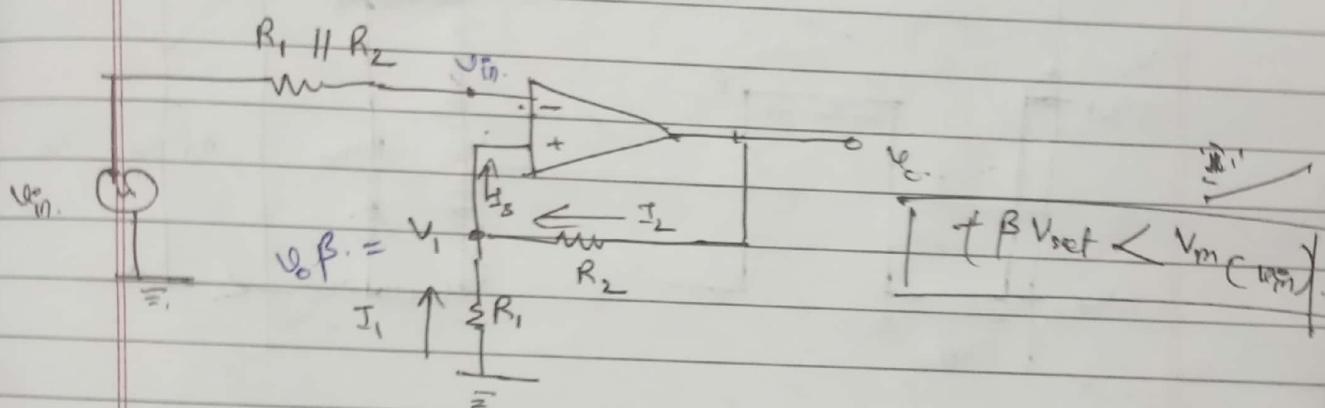

Apply KCL at ptn ③.

$$I_1 + I_2 = I_3 = 0$$

$$\frac{0 - V_1}{R_1} + \frac{V_o - V_1}{R_2} = 0$$

$$\frac{V_o}{R_2} = V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V_o = V_1 \left( \frac{R_1 + R_2}{R_1} \right)$$

$$V_1 = \left( \frac{R_1}{R_1 + R_2} \right) V_o$$

$\beta$ .

$+V_{set}$        $UTV \rightarrow$  upper threshold voltage  
 $-V_{set}$        $LTV \rightarrow$  lower

DATE: / /  
PAGE: \_\_\_\_\_



Assume  $V_b = +V_{set}$ .

then  $V_i = \beta V_{set}$ .


Now  $V_b = -V_{set}$ .

then  $V_i = -\beta V_{set}$ .


Square wave converter.

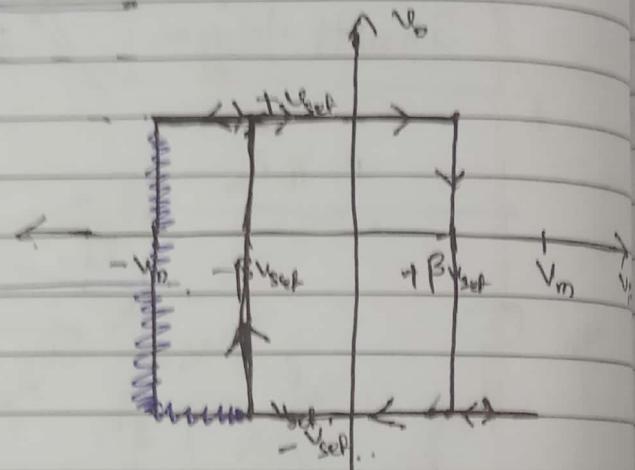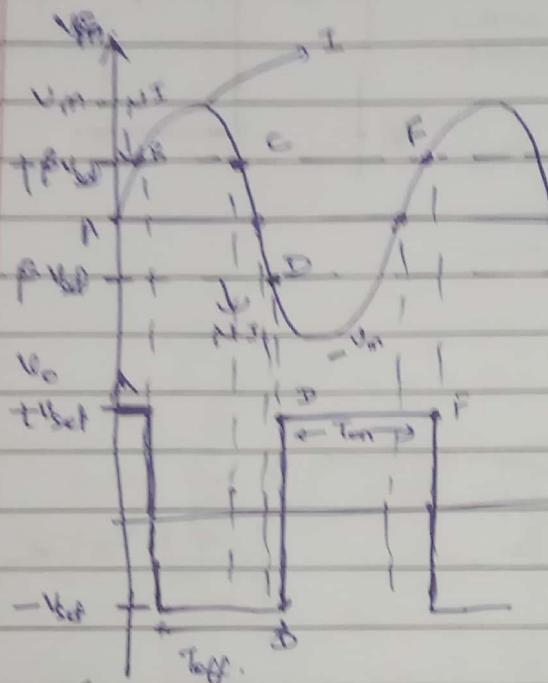

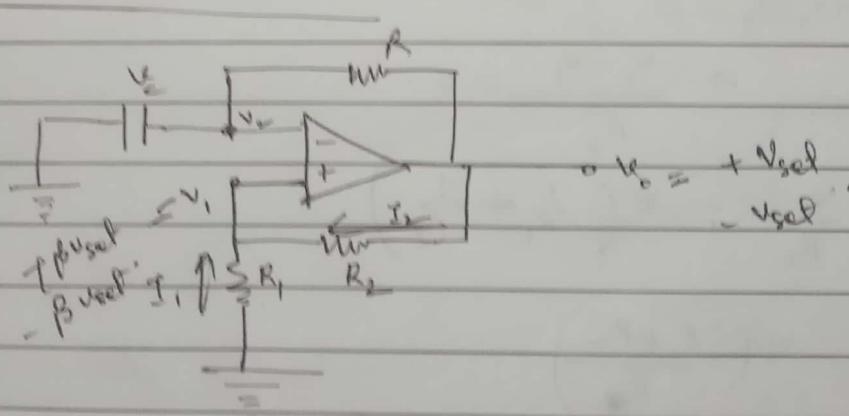~~11/11/19~~ Square wave Generator - (non-sinusoidal oscillator).



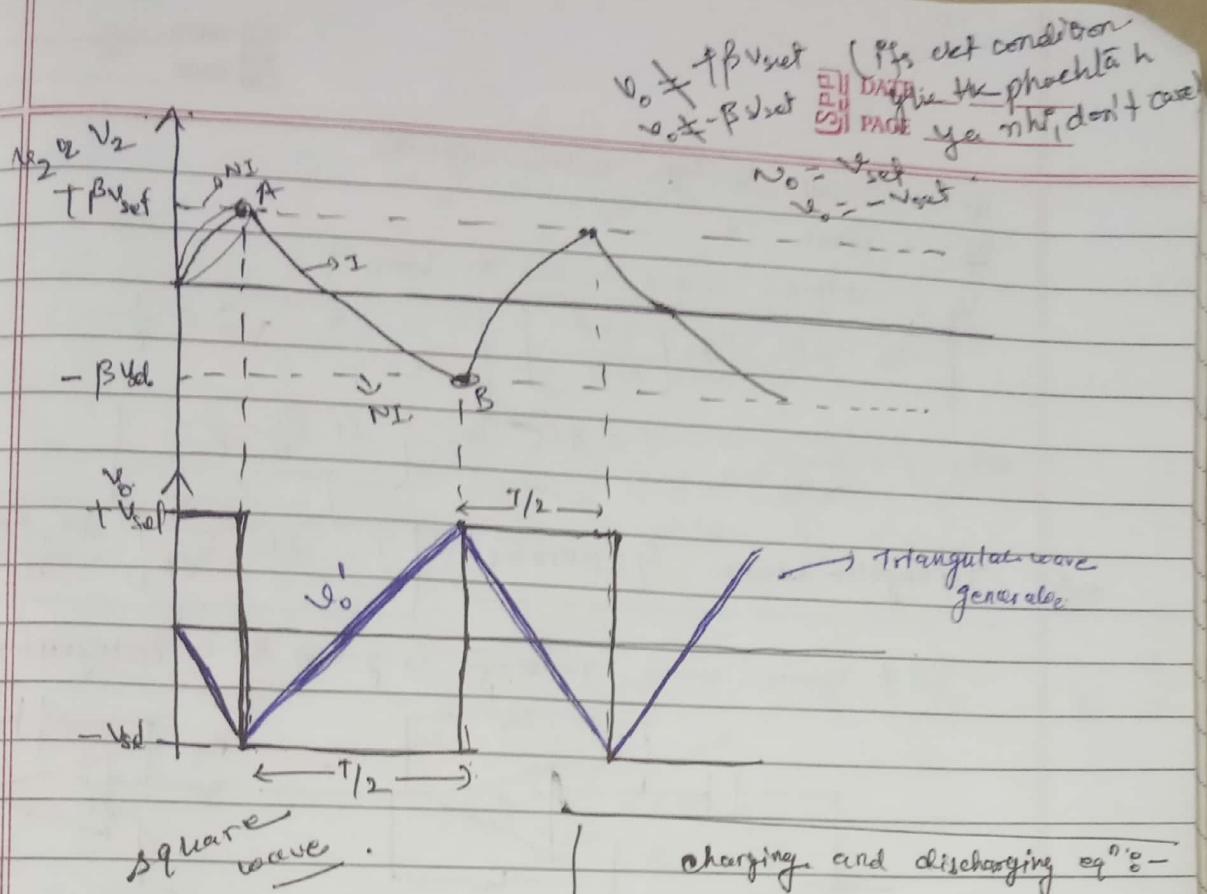- \* op-amp is forced to operate in saturation region.
- \* Initially capacitor is fully discharged.



Apply KCL at pin ③

$$I_1 + I_2 = 0$$

$$\frac{0 - V_i}{R_1} + \frac{V_o - V_i}{R_2} = 0$$

$$\frac{V_o}{R_2} = \frac{V_i}{R_1} + \frac{V_i}{R_2}$$

$$\frac{V_o}{R_2} = V_i \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V_o = V_i \left( \frac{R_1 + R_2}{R_1} \right)$$

$$V_i = \beta V_o$$

$$V_i = \beta V_o$$

$$\text{If } V_o = +V_{set}$$

$$\text{then } V_i = +\beta V_{set}$$

$$\text{If } V_o = -V_{set}$$

$$\text{then } V_i = -\beta V_{set}$$

for single time constant RC Ckt :-

$$V_t = V_f + (V_i - V_f) e^{-t/RC}$$

During Discharging :- A.B.

$$V_i = +\beta V_{set}$$

$$V_f = -V_{set}$$

$$\text{at } t = T/2$$

$$V_t = -\beta V_{set}$$

Put in ①

$$-\beta V_{set} = -V_{set} + (\beta V_{set} + V_{set}) e^{-T/2RC}$$

$$\beta V_{set} (1 - \beta) = V_{set} (1 + \beta) e^{-T/2RC}$$

$$\frac{1 - \beta}{1 + \beta} = e^{-T/2RC}$$

frequency

$$e^{T/2RC} = \frac{1 + \beta}{1 - \beta}$$

$v_0 \rightarrow$  Initial Voltage across capacitors

$v_f \rightarrow$  final " " "

$V_t =$  Voltage across across at time t.


$$T = 2RC \log_e \left[ \frac{1+\beta}{1-\beta} \right] \quad \text{and} \quad \beta = \frac{1}{T}$$

$$\text{also, } \beta = \frac{R_1}{R_1 + R_2}, \quad T = 2RC \log_e \left[ \frac{1 + \frac{R_1}{R_1 + R_2}}{1 - \frac{R_1}{R_1 + R_2}} \right]$$

$\Rightarrow$  Triangular wave Generator

$$T = 2RC \log_e \left[ \frac{2R_1 + R_2}{R_2} \right]$$

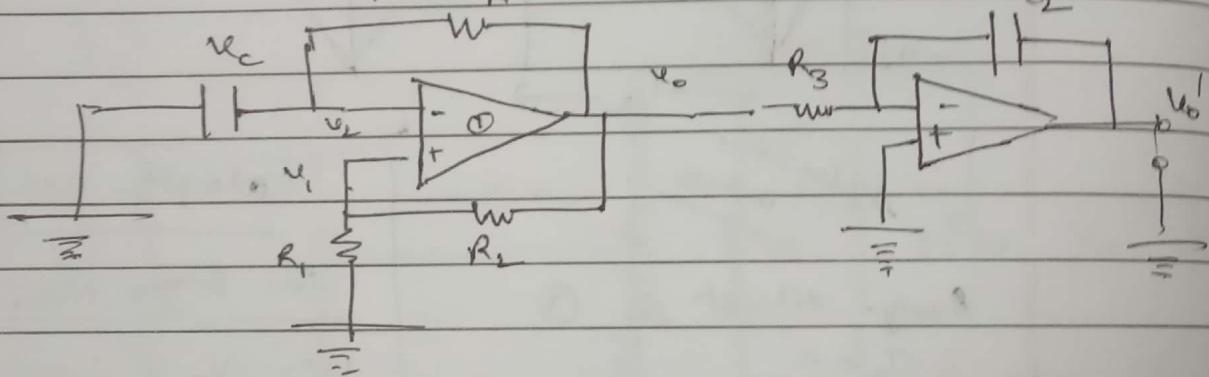OP of square wave generator is given to a Integrator ckt.



$V_i \rightarrow$  Initial Voltage across capacitors.

$V_f \rightarrow$  final " " "

$V_t =$  Voltage across across at time t.

$$T = 2RC \log_e \left[ \frac{1+\beta}{1-\beta} \right]$$


$$\beta = \frac{1}{T}$$

also,  $\beta = \frac{R_1}{R_1 + R_2}$ ,  $T = 2RC \log_e \left[ \frac{1 + \frac{R_1}{R_1 + R_2}}{1 - \frac{R_1}{R_1 + R_2}} \right]$

$\Rightarrow$  Triangular wave Generator

$$T = 2RC \log_e \left[ \frac{2R_1 + R_2}{R_2} \right]$$

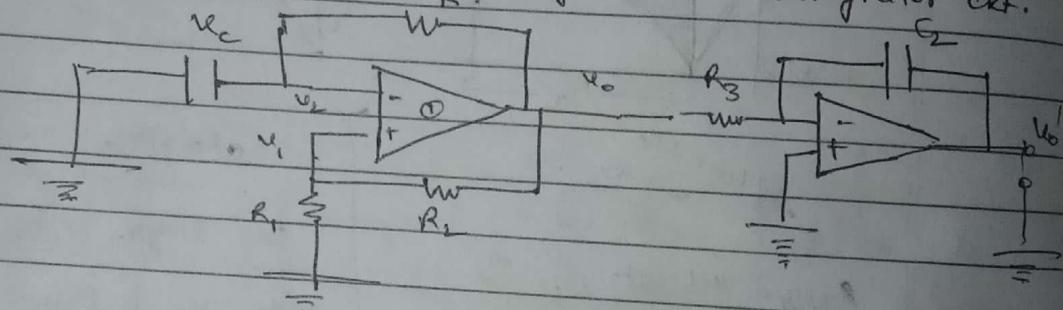OP of square wave generator is given by a Integrator ckt.




21/11/19

Active filter :-

OP is obtained  
v signal.

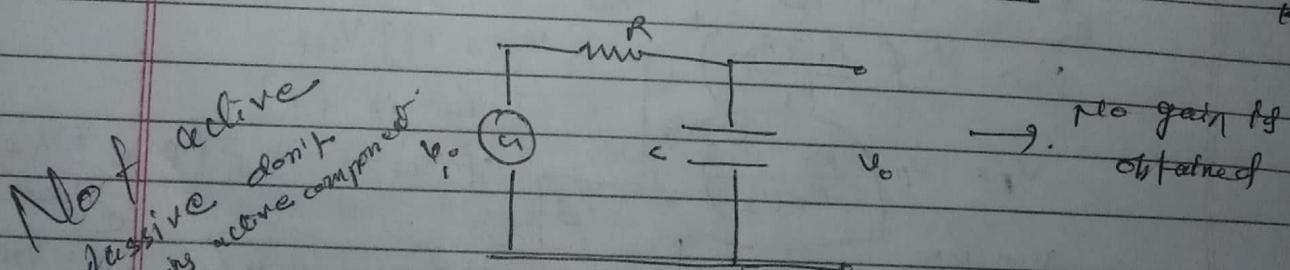II low pass filter (low pass ckt) —  
allows low & blocks high  
two opp.



No active  
passive, don't  
contains active component

at low freq.

$$X_C = \frac{1}{2\pi f C}$$

f → high

$$F = \infty$$


$X_C = 0 \rightarrow$  short ckt.

$$V_o = 0$$

$X_C = \infty \rightarrow$  open ckt.


$$V_o = V_i$$

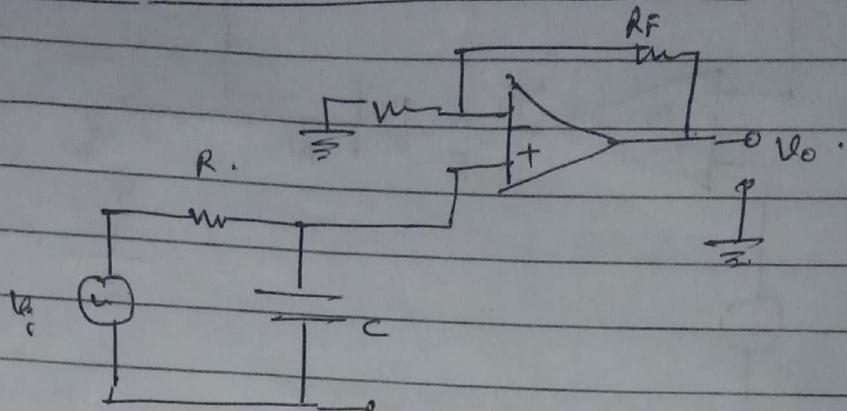1<sup>st</sup> order low pass active low pass filter -



High pass filter:-

passive

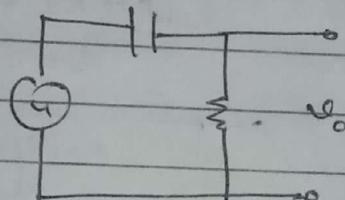

$$X_C = \frac{1}{2\pi f C}$$

at low freq.

$f \rightarrow 0$

$X_C = \infty$

$C \rightarrow 0$

$V_o = 0$

at high f


$f \rightarrow \infty$

$X_C = 0$


$C \rightarrow \infty$

$V_o = V_{o0}$

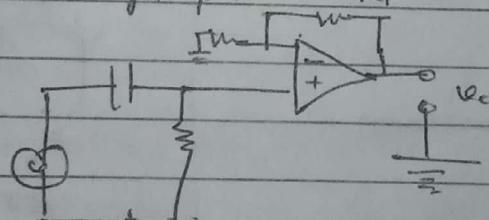1<sup>st</sup> order active high pass C/HF: RF



- for low voltage I/P signal

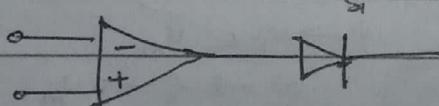

Precision diode .

half wave rectifier can't  
rectify low voltage

signal like mV or nV

let  $A_V \rightarrow$  very high ( $10^4$ )

bcz  $V_T = 0.6V$  for Si

$$A_V = \frac{off}{I/P} = 10^4$$

the Diode will never  
conduct & no off  
will be obtained.

$$\frac{D.C}{I/P} = 10^4$$


$I/P = 0.6 \times 10^{-4} V$  .  $\rightarrow$  I/P signal should be greater  
than 60 mV .

$= 60 \text{ mV} \rightarrow$  minimum voltage (at least)

GOOD WRITE

# Precision rectifier using diode

DATE: \_\_\_\_\_  
PAGE \_\_\_\_\_

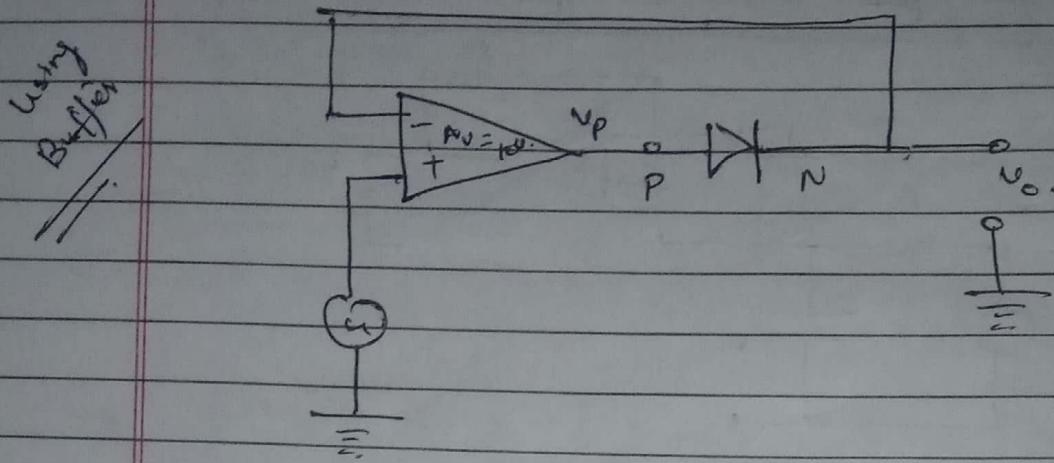

If  $v_i > 60 \text{ mV}$

$$v_p > 0.6 \text{ V}$$

$\rightarrow D \rightarrow PB \rightarrow SC$


$$v_o = v_i$$

If  $v_i < 60 \text{ mV}$

$$v_p < 0.6 \text{ V}$$

$\rightarrow D \rightarrow RB \rightarrow OC$

$$v_o = 0$$

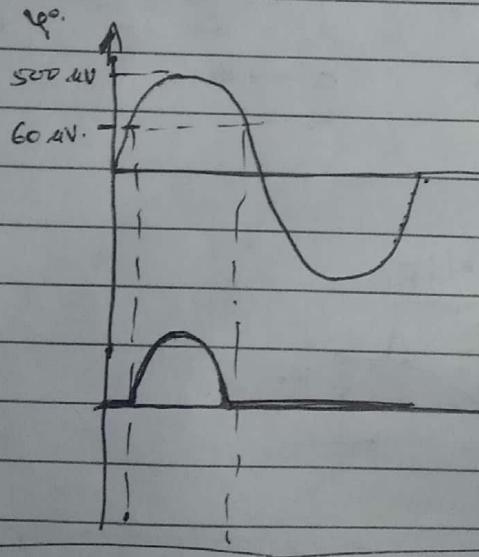

Multimeter  $\rightarrow$  only measures sine wave  
can't use for measuring other signals peak value.

## Peak Defector:-




$\downarrow$  sin, cos, square, triangle  
 $\downarrow$  non-sinusoidal signals

for high I/P signal.

$$P \rightarrow v_p < v_m$$

$$N \rightarrow v_c \rightarrow v_m$$

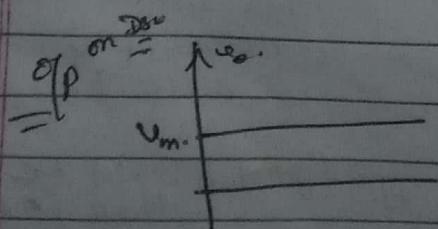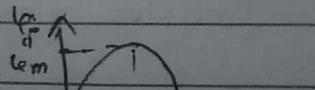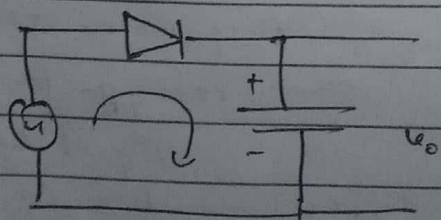
$\rightarrow D \rightarrow RB \rightarrow OC$




$D_{SO} \leftarrow$   
don't show

GOOD WRITE

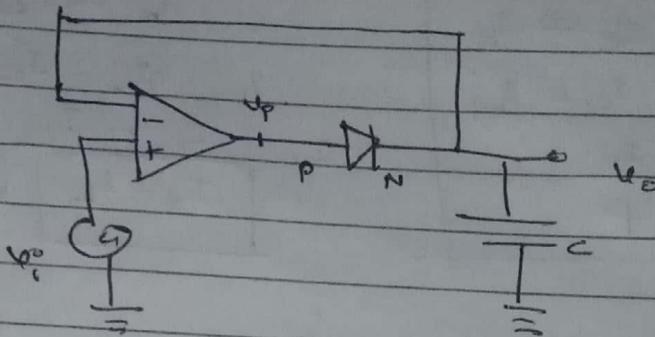Peak Detector  $\rightarrow$  for low signal  $\rightarrow$  Precision diode



\* Current mirror. / 8-- .

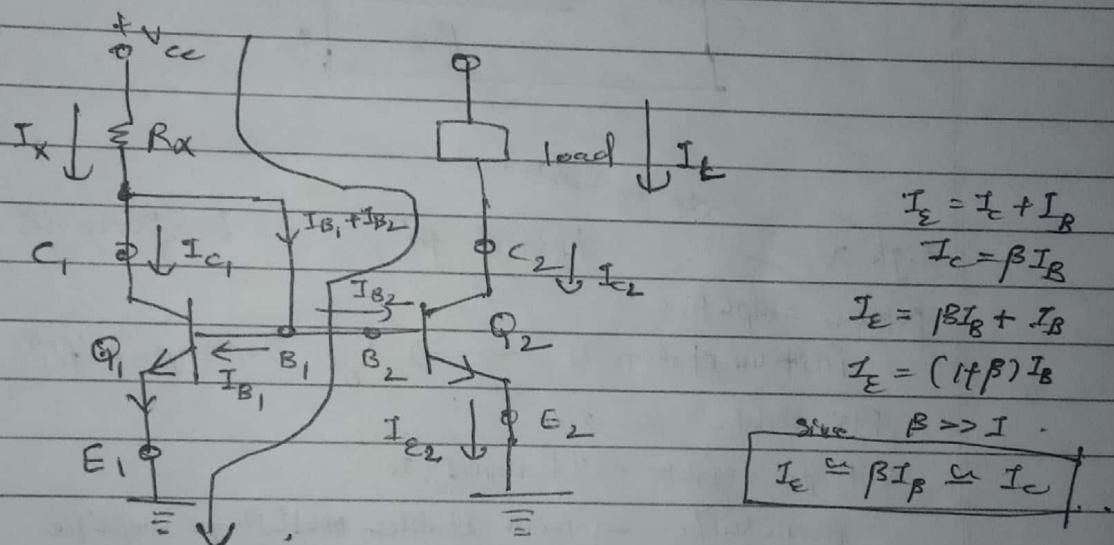

- ① Both transistors are identical.  
② Both transistors are in active region.

$$I_L = I_{C_2}$$

Since both transistors are identical.

$$V_{BE1} = V_{BE2}$$

$$I_{B_1} = I_{B_2} = I_B$$

$$I_{\varepsilon_1} = I_{\varepsilon_2} = I_{\varepsilon} \quad \checkmark$$

$$\Rightarrow I_x = I_{C_1} + I_{B_1} + I_{B_2}$$

$$= I_{C_1} + 2I_B = I_{E_1} + 2I_B = I_E + 2I_B$$

$$I_x = I_e + 2 \frac{I_e}{\beta} = I_e \left( 1 + \frac{2}{\beta} \right)$$

**GOOD WRITE**

$$I_x = I_\infty \Rightarrow I_x = I_c$$

since  $\beta \rightarrow$  large

$$\text{since, } I_C \approx I_E$$

$$I_{C1} = I_{E1}$$

$$I_E \approx \beta I_B, \Rightarrow I_B = \frac{I_E}{\beta}$$

$$I_X \approx I_C$$

$$I_{C1} = I_{C2} = I_C$$

$$I_X = I_{C2} = I_L$$

$$I_X = I_L$$

Apply KVL on I/p.

$$V_{CC} - I_X R_X - V_{BE} = 0$$

$$I_X = \frac{V_{CC} - V_{BE}}{R_X}$$

do by ~~usset~~

high  $V$   $\rightarrow$  hybrid  $\pi^o$ ,  $h$ -parameter  $\rightarrow$  low  $V$ .

power amplifier

Instrumentation  $\rightarrow$  by 8 opamp diff'nt ampli ✓

PIV rectifier  $\rightarrow$

voltage regulator  $\rightarrow$  3 terminal IC.

monostab.  $\rightarrow$  mono & stable multistage amplifier.